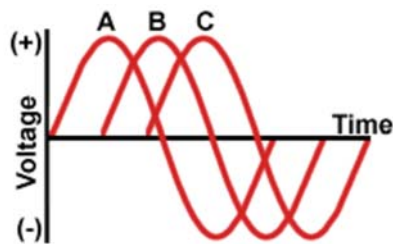


Chapter 12


Three-Phase Circuits



Power Factor Correction




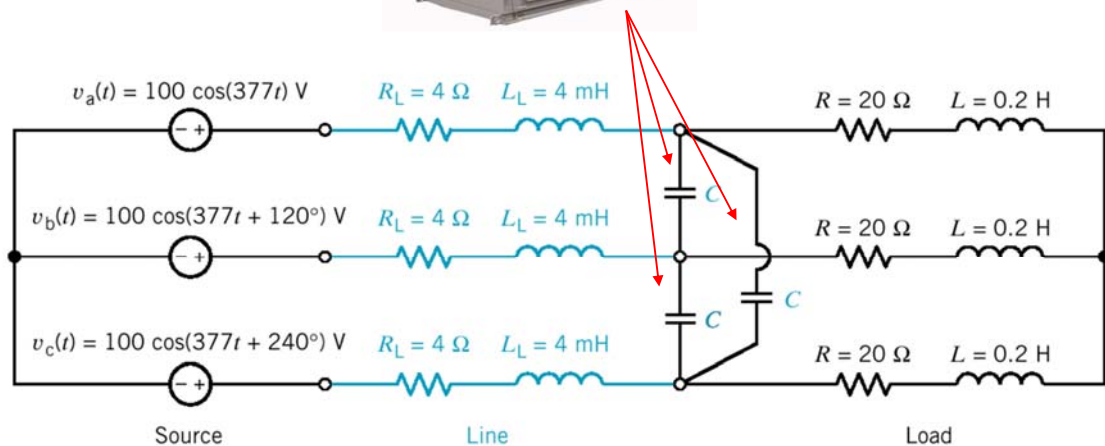**Medium Voltage Metal
Enclosed Capacitor Banks**




A balanced three-phase circuit

Three-Phase Voltages

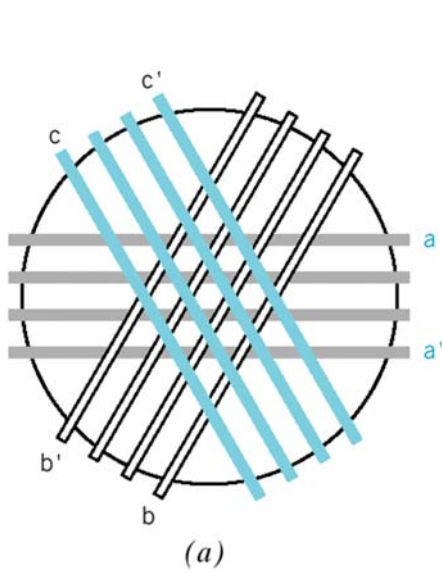

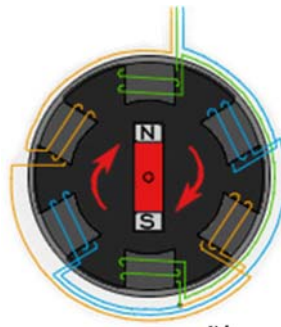
(a) The three windings on a cylindrical drum used to obtain three-phase voltages



$$v_{aa'} = \sqrt{2} V \cos \omega t$$


$$v_{bb'} = \sqrt{2} V \cos(\omega t - 120^\circ)$$
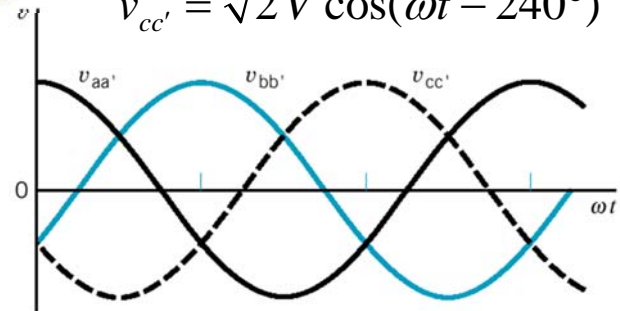
$$v_{cc'} = \sqrt{2} V \cos(\omega t - 240^\circ)$$




(b) Balanced three-phase voltages

Three-Phase Voltages

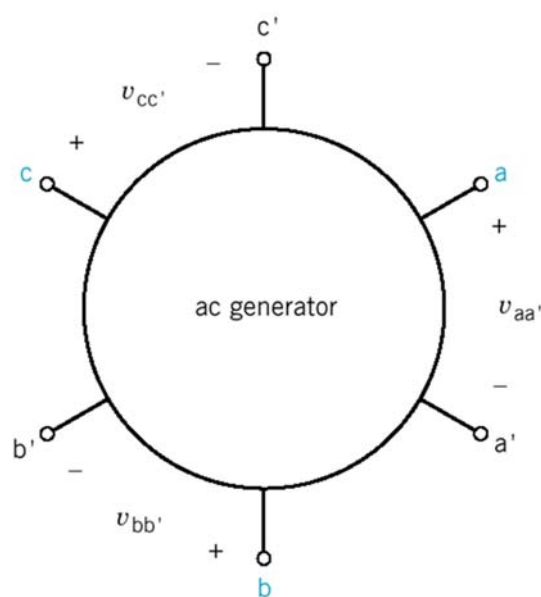

Generator with six terminals

Three-Phase Balanced Voltages

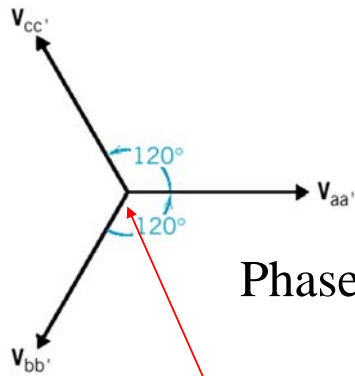


$$V_{aa'} = V \angle 0^\circ$$

$$V_{bb'} = V \angle -120^\circ$$

$$V_{cc'} = V \angle -240^\circ = V \angle +120^\circ$$

Phase sequence or phase rotation is **abc**
Positive Phase Sequence

neutral terminal

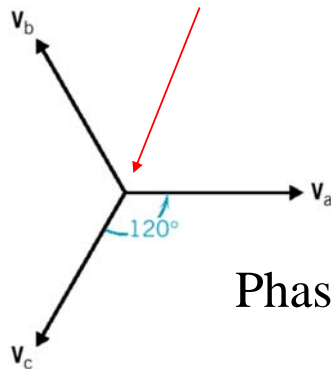


$$V_a = V \angle 0^\circ$$

$$V_c = V \angle -120^\circ$$


$$V_b = V \angle -240^\circ = V \angle +120^\circ$$

Phase sequence or phase rotation is **acb**
Negative Phase Sequence

Two Common Methods of Connection

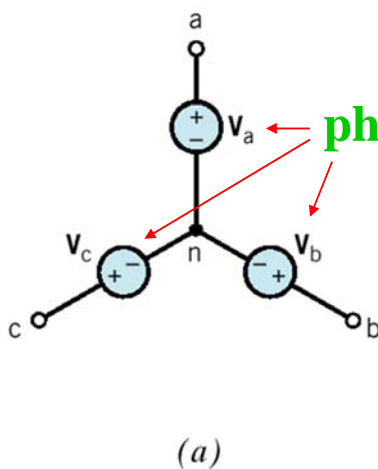


(a)

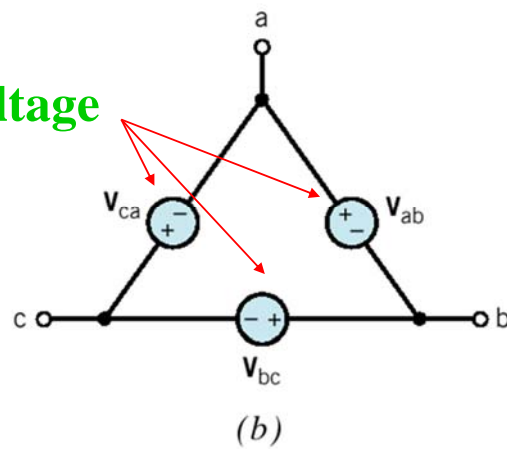

(b)

(a) Y-connected sources (b) Δ -connected sources

Phase and Line Voltages

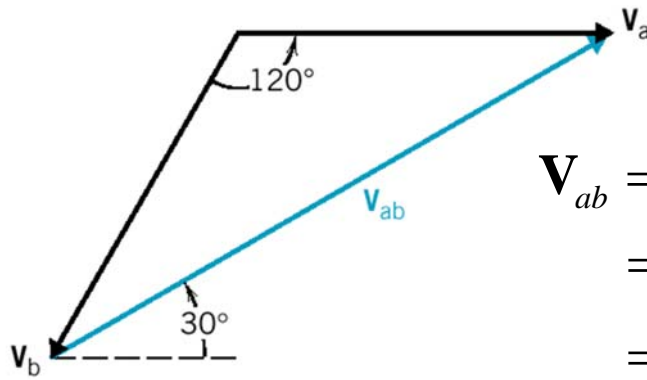

$$\begin{aligned}
 \mathbf{V}_{ab} &= \mathbf{V}_a - \mathbf{V}_b \\
 &= V_p \angle 0^\circ - V_p \angle -120^\circ \\
 &= V_p - V_p(-0.5 - j0.866) \\
 &= \sqrt{3}V_p \angle 30^\circ
 \end{aligned}$$


The line-to-line voltage \mathbf{V}_{ab} of the Y-connected source

Similarly

$$\mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ$$

$$\mathbf{V}_{ca} = \sqrt{3}V_p \angle -210^\circ$$

The Y-to-Y Circuit

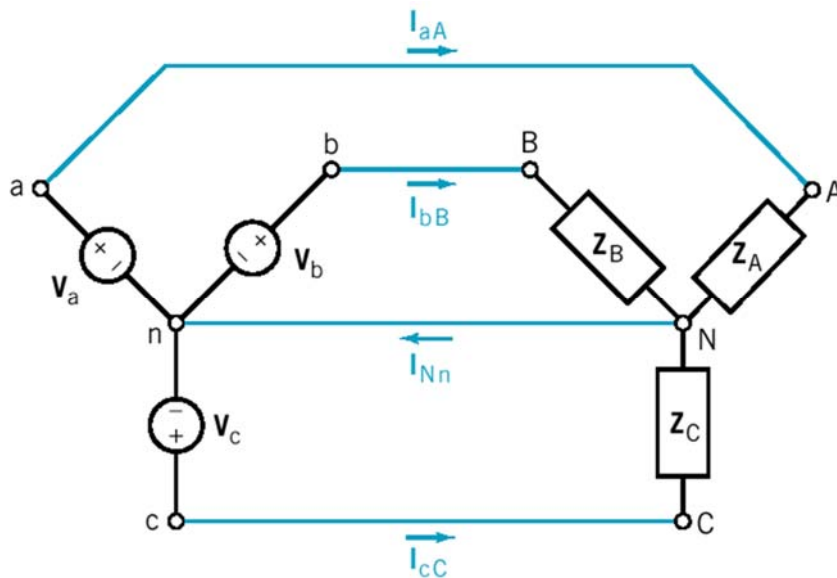

A four-wire Y-to-Y circuit

The Y-to-Y Circuit (cont.)

Four - wire

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_A}, \mathbf{I}_{bB} = \frac{\mathbf{V}_b}{\mathbf{Z}_B}, \text{ and } \mathbf{I}_{cC} = \frac{\mathbf{V}_c}{\mathbf{Z}_C}$$

$$\mathbf{I}_{nN} = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC}$$

The average power delivered by the three-phase source to the three-phase load

$$P = P_A + P_B + P_C$$

When $\mathbf{Z}_A = \mathbf{Z}_B = \mathbf{Z}_C$ the load is said to be *balanced*

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_A} = \frac{V \angle 0^\circ}{Z \angle \theta}, \mathbf{I}_{bB} = \frac{\mathbf{V}_b}{\mathbf{Z}_B} = \frac{V \angle -120^\circ}{Z \angle \theta}, \text{ and } \mathbf{I}_{cC} = \frac{\mathbf{V}_c}{\mathbf{Z}_C} = \frac{V \angle 120^\circ}{Z \angle \theta}$$

$$\mathbf{I}_{aA} = \frac{V}{Z} \angle -\theta^\circ, \mathbf{I}_{bB} = \frac{V}{Z} \angle (-\theta - 120^\circ), \text{ and } \mathbf{I}_{cC} = \frac{V}{Z} \angle (-\theta + 120^\circ)$$

The Y-to-Y Circuit(cont.)

There is no current in the wire connecting the neutral node of the source to the neutral node of the load.

$$\mathbf{I}_{nN} = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 0$$


The average power delivered to the load is

$$P = P_A + P_B + P_C$$

$$= V \frac{V}{Z} \cos(-\theta) + V \frac{V}{Z} \cos(-\theta) + V \frac{V}{Z} \cos(-\theta)$$

$$= 3 \frac{V^2}{Z} \cos(\theta)$$

The Y-to-Y Circuit (cont.)

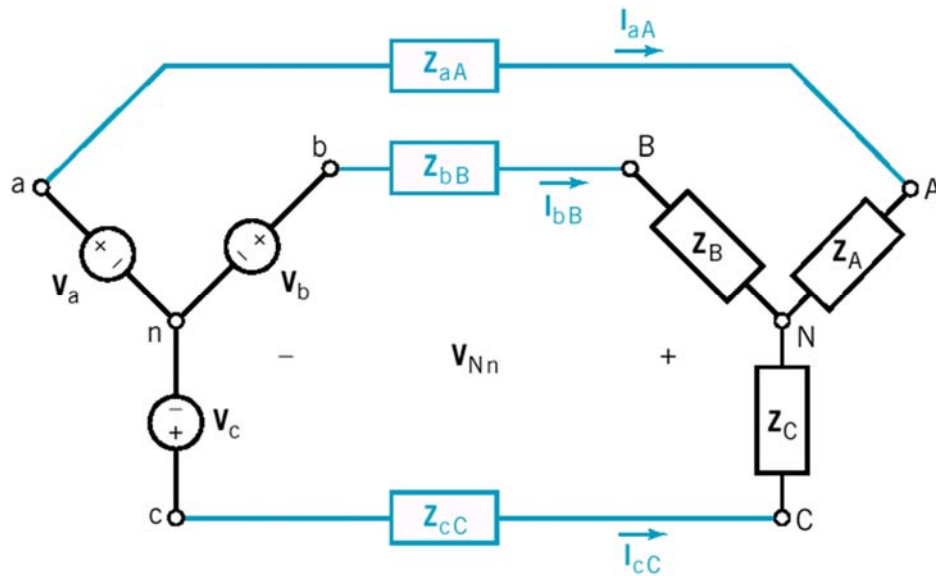

A three-wire Y-to-Y circuit

The Y-to-Y Circuit (cont.)

Three - wire

We need to solve for V_{Nn}

$$\begin{aligned}
 0 &= \frac{V_a - V_{Nn}}{Z_A} + \frac{V_b - V_{Nn}}{Z_B} + \frac{V_c - V_{Nn}}{Z_C} \\
 &= \frac{V \angle 0^\circ - V_{Nn}}{Z_A} + \frac{V \angle -120^\circ - V_{Nn}}{Z_B} + \frac{V \angle 120^\circ - V_{Nn}}{Z_C}
 \end{aligned}$$

Solve for V_{Nn}

$$V_{Nn} = \frac{(V \angle -120^\circ) Z_A Z_C + V \angle 120^\circ Z_A Z_B + V \angle 0^\circ Z_B Z_C}{Z_A Z_C + Z_A Z_B + Z_B Z_C}$$

$$I_{aA} = \frac{V_a - V_{Nn}}{Z_A}, I_{bB} = \frac{V_b - V_{Nn}}{Z_B}, \text{ and } I_{cC} = \frac{V_c - V_{Nn}}{Z_C}$$

The Y-to-Y Circuit (cont.)

When the circuit is **balanced** i.e. $\mathbf{Z}_A = \mathbf{Z}_B = \mathbf{Z}_C$

$$\mathbf{V}_{Nn} = \frac{(V \angle -120^\circ)\mathbf{Z} + V \angle 120^\circ\mathbf{Z} + V \angle 0^\circ\mathbf{Z}}{\mathbf{Z} + \mathbf{Z} + \mathbf{Z}}$$


$$= 0$$

The average power delivered to the load is

$$P = P_A + P_B + P_C$$

$$= 3 \frac{V^2}{Z} \cos(\theta)$$

The Y-to-Y Circuit (cont.)

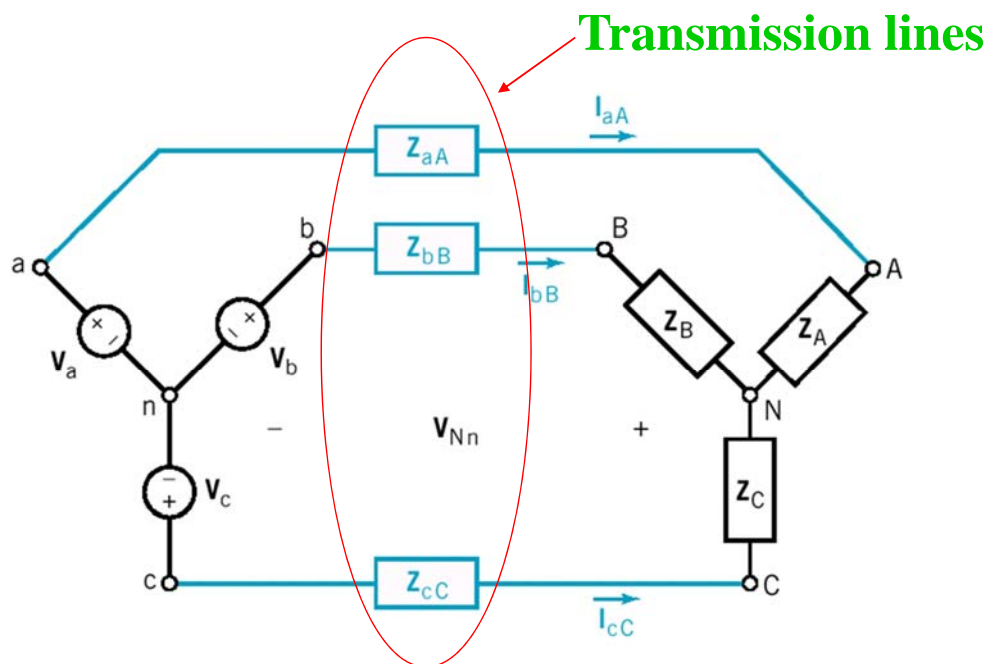


A three-wire Y-to-Y circuit with line impedances

The Y-to-Y Circuit (cont.)


The analysis of *balanced Y-Y circuits* is *simpler* than the analysis of *unbalanced Y-Y circuits*.

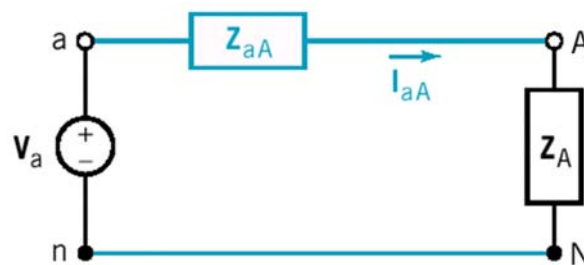- ✚ $V_{Nn} = 0$. It is not necessary to solve for V_{Nn} .
- ✚ The line currents have equal magnitudes and differ in phase by 120 degree.
- ✚ Equal power is absorbed by each impedance.



Per-phase equivalent circuit

Example 12.4-1 $S = ?$

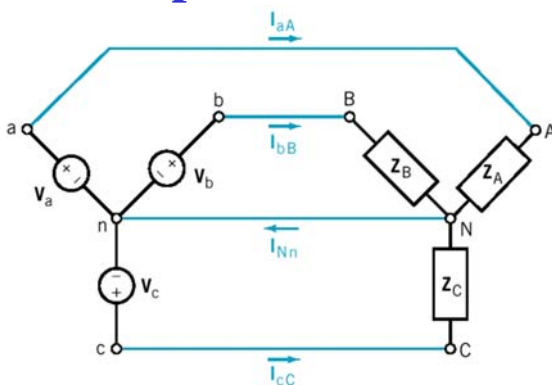

Unbalanced 4-wire

$$\begin{aligned} \mathbf{V}_a &= 110\angle 0^\circ \quad \mathbf{V}_{\text{rms}} \\ \mathbf{V}_b &= 110\angle -120^\circ \quad \mathbf{V}_{\text{rms}} \\ \mathbf{V}_c &= 110\angle 120^\circ \quad \mathbf{V}_{\text{rms}} \\ \mathbf{Z}_A &= 50 + j80 \quad \Omega \\ \mathbf{Z}_B &= j50 \quad \Omega \\ \mathbf{Z}_C &= 100 + j25 \quad \Omega \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{aA} &= \frac{\mathbf{V}_a}{\mathbf{Z}_A} = \frac{110\angle 0^\circ}{50 + j80} = 1.16\angle -58^\circ \quad \text{A}_{\text{rms}} \\ \mathbf{I}_{bB} &= \frac{\mathbf{V}_b}{\mathbf{Z}_B} = \frac{110\angle -120^\circ}{j50} = 2.2\angle 150^\circ \quad \text{A}_{\text{rms}} \\ \mathbf{I}_{cC} &= \frac{\mathbf{V}_c}{\mathbf{Z}_C} = \frac{110\angle 120^\circ}{100 + j25} = 1.07\angle -106^\circ \quad \text{A}_{\text{rms}} \end{aligned}$$

Example 12.4-1 (cont.)

$$\mathbf{S}_A = \mathbf{I}_{aA}^* \mathbf{V}_a = 68 + j109 \quad \text{VA}$$

$$\mathbf{S}_B = \mathbf{I}_{bB}^* \mathbf{V}_b = j242 \quad \text{VA}$$

$$\mathbf{S}_C = \mathbf{I}_{cC}^* \mathbf{V}_c = 114 + j28 \quad \text{VA}$$

The total complex power delivered to the three-phase load is

$$\mathbf{S} = \mathbf{S}_A + \mathbf{S}_B + \mathbf{S}_C = 182 + j379 \quad \text{VA}$$

Example 12.4-2 $\mathbf{S} = ?$ Balanced 4-wire

$$\mathbf{V}_a = 110 \angle 0^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_A = 50 + j80 \quad \Omega$$

$$\mathbf{V}_b = 110 \angle -120^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_B = 50 + j80 \quad \Omega$$

$$\mathbf{V}_c = 110 \angle 120^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_C = 50 + j80 \quad \Omega$$

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_A} = \frac{110 \angle 0^\circ}{50 + j80} = 1.16 \angle -58^\circ \quad \text{A}_{\text{rms}}$$

$$\mathbf{S}_A = \mathbf{I}_{aA}^* \mathbf{V}_a = 68 + j109 \quad \text{VA}$$

The total complex power delivered to the three-phase load is

$$\mathbf{S} = 3\mathbf{S}_A = 204 + j326 \quad \text{VA}$$

Also

$$\mathbf{I}_{bB} = 1.16 \angle -177^\circ \quad \text{A}_{\text{rms}}, \mathbf{I}_{cC} = 1.16 \angle 62^\circ \quad \text{A}_{\text{rms}}$$

$$\mathbf{S}_B = 68 + j109 \quad \text{VA} = \mathbf{S}_C$$

Example 12.4-3 **S = ?**

$$\mathbf{V}_a = 110\angle 0^\circ \quad \mathbf{V}_{\text{rms}}$$


$$\mathbf{V}_b = 110\angle -120^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_c = 110\angle 120^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{Z}_A = 50 + j80 \quad \Omega$$

$$\mathbf{Z}_B = j50 \quad \Omega$$

$$\mathbf{Z}_C = 100 + j25 \quad \Omega$$

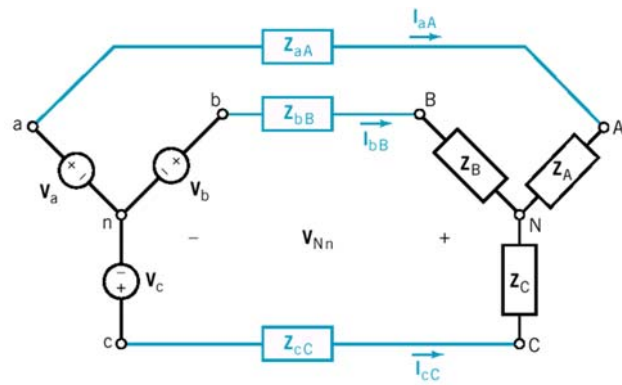

Unbalanced 3-wire

Determine \mathbf{V}_{Nn}

$$\mathbf{V}_{Nn} = \frac{(110\angle -120^\circ)\mathbf{Z}_A\mathbf{Z}_C + 110\angle 120^\circ\mathbf{Z}_A\mathbf{Z}_B + 110\angle 0^\circ\mathbf{Z}_B\mathbf{Z}_C}{\mathbf{Z}_A\mathbf{Z}_C + \mathbf{Z}_A\mathbf{Z}_B + \mathbf{Z}_B\mathbf{Z}_C}$$

$$= 56\angle -151^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a - \mathbf{V}_{Nn}}{\mathbf{Z}_A}, \mathbf{I}_{bB} = \frac{\mathbf{V}_b - \mathbf{V}_{Nn}}{\mathbf{Z}_B}, \text{ and } \mathbf{I}_{cC} = \frac{\mathbf{V}_c - \mathbf{V}_{Nn}}{\mathbf{Z}_C}$$

Example 12.4-3 (cont.)

$$\mathbf{I}_{aA} = 1.71\angle -48^\circ, \mathbf{I}_{bB} = 2.45\angle 3^\circ, \text{ and } \mathbf{I}_{cC} = 1.19\angle 79^\circ$$

$$\mathbf{S}_A = \mathbf{I}_{aA}^* \mathbf{V}_a = \mathbf{I}_{aA}^* (\mathbf{I}_{aA} \mathbf{Z}_A) = 146 + j234 \quad \text{VA}$$

$$\mathbf{S}_B = \mathbf{I}_{bB}^* \mathbf{V}_b = \mathbf{I}_{bB}^* (\mathbf{I}_{bB} \mathbf{Z}_B) = j94 \quad \text{VA}$$

$$\mathbf{S}_C = \mathbf{I}_{cC}^* \mathbf{V}_c = \mathbf{I}_{cC}^* (\mathbf{I}_{cC} \mathbf{Z}_C) = 141 + j35 \quad \text{VA}$$

The total complex power delivered to the three-phase load is

$$\mathbf{S} = \mathbf{S}_A + \mathbf{S}_B + \mathbf{S}_C = 287 + j364 \quad \text{VA}$$

Example 12.4-4 $S = ?$ Balanced 3-wire

$$\mathbf{V}_a = 110\angle 0^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_A = 50 + j80 \quad \Omega$$

$$\mathbf{V}_b = 110\angle -120^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_B = 50 + j80 \quad \Omega$$

$$\mathbf{V}_c = 110\angle 120^\circ \quad \mathbf{V}_{\text{rms}} \qquad \mathbf{Z}_C = 50 + j80 \quad \Omega$$



$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_A} = \frac{110\angle 0^\circ}{50 + j80} = 1.16\angle -58^\circ \quad \text{A}_{\text{rms}}$$

$$\mathbf{S}_A = \mathbf{I}_{aA}^* \mathbf{V}_a = 68 + j109 \quad \text{VA}$$

The total complex power delivered to the three-phase load is

$$\mathbf{S} = 3\mathbf{S}_A = 204 + j326 \quad \text{VA}$$

Example 12.4-5 $P_{\text{Load}} = ?$ $P_{\text{Line}} = ?$ $P_{\text{Source}} = ?$

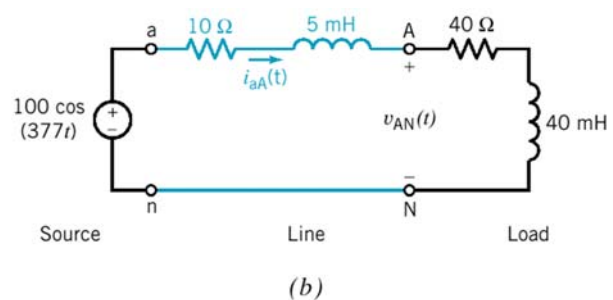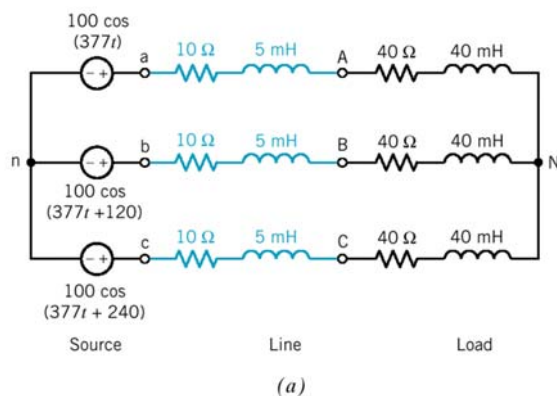

Balanced 3-wire

**per-phase
equivalent circuit**

$$\mathbf{I}_{aA}(\omega) = \frac{\mathbf{V}_a}{\mathbf{Z}_A} = \frac{100\angle 0^\circ}{50 + j(377)(0.045)} = 1.894\angle -18.7^\circ \quad \text{A}$$

The phase voltage at the load is

$$\mathbf{V}_{AN}(\omega) = (40 + j(377)(0.04))\mathbf{I}_{aA}(\omega) = 81\angle 2^\circ \quad \text{V}$$

Example 12.4-5 (cont.)

The power delivered by the source is

$$\begin{aligned} P_a &= \frac{V_m I_m}{2} \cos(\theta_V - \theta_I) \\ &= \frac{(100)(1.894)}{2} \cos(18.7^\circ) = 89.7 \text{ W} \end{aligned}$$

The power delivered to the load is


$$P_A = \frac{I_m^2}{2} \operatorname{Re}(\mathbf{Z}_A) = \frac{(1.894)^2}{2} 40 = 71.7 \text{ W}$$

The power lost in the line is

$$P_{aA} = \frac{I_m^2}{2} \operatorname{Re}(\mathbf{Z}_{Line}) = \frac{(1.894)^2}{2} 10 = 17.9 \text{ W}$$

Line loss $\approx 20\%$

The Δ -Connected Source and Load

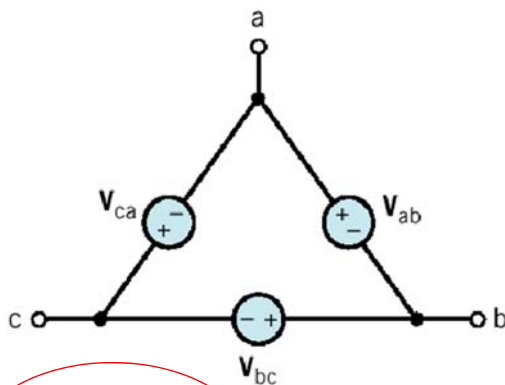

$$\mathbf{V}_{ab} = 120 \angle 0^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_{bc} = 120.1 \angle -121^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_{ca} = 120.2 \angle 121^\circ \quad \mathbf{V}_{\text{rms}}$$

Circulating
current


$$\mathbf{I} = \frac{(\mathbf{V}_{ab} + \mathbf{V}_{bc} + \mathbf{V}_{ca})}{1} \approx -3.75 \text{ A}$$

Unacceptable

Total resistance around the loop

Therefore the Δ sources connection is seldom used in practice.


The Δ -Y and Y- Δ Transformation

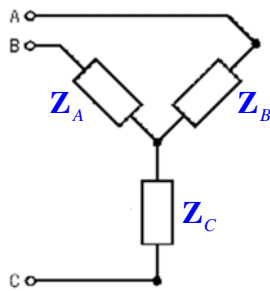

$$Z_A = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_B = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$
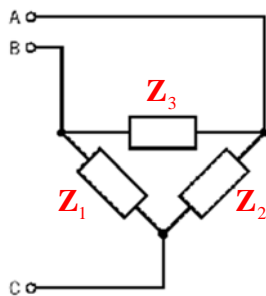
$$Z_C = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$




$$Z_1 = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_B}$$


$$Z_2 = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_A}$$

$$Z_3 = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_C}$$


Example

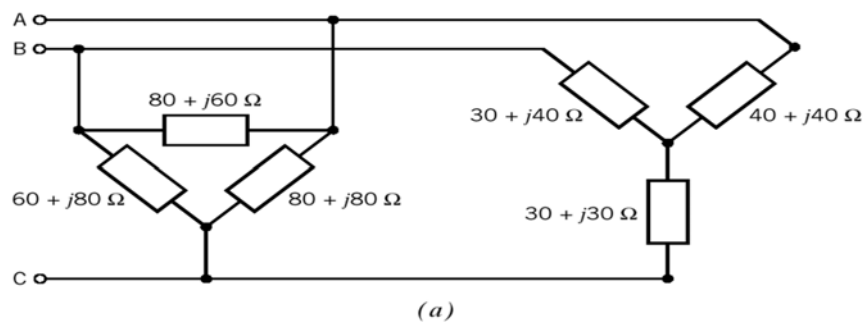


(a)

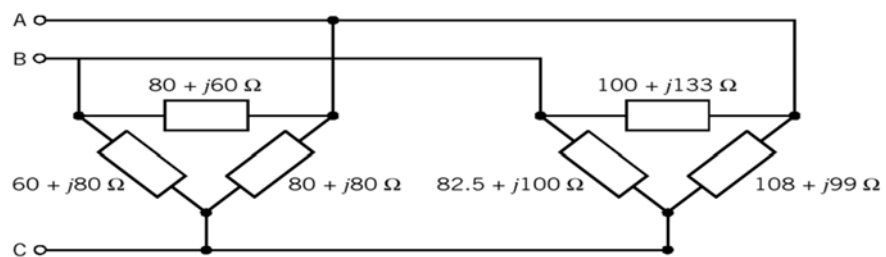

(b)

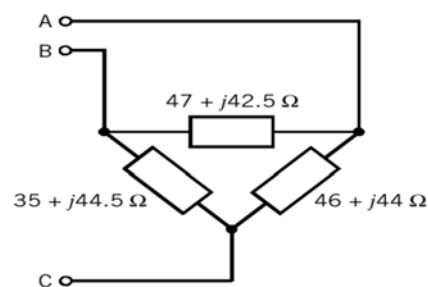


(c)

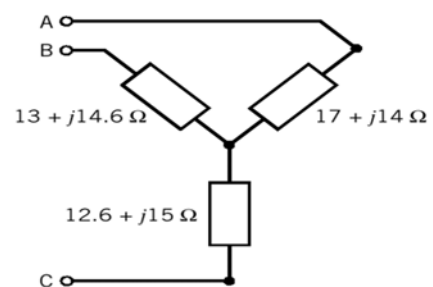

(d)

The Y- Δ Circuits

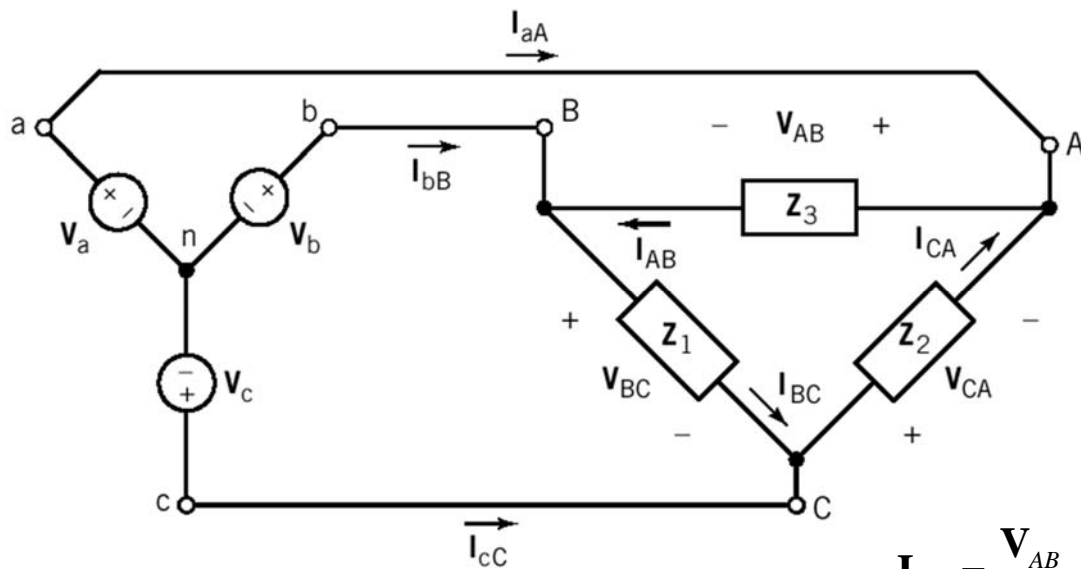

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

$$\mathbf{I}_{bB} = \mathbf{I}_{BC} - \mathbf{I}_{AB}$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$


where

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_3}$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_1}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_2}$$

The Y- Δ Circuits (cont.)

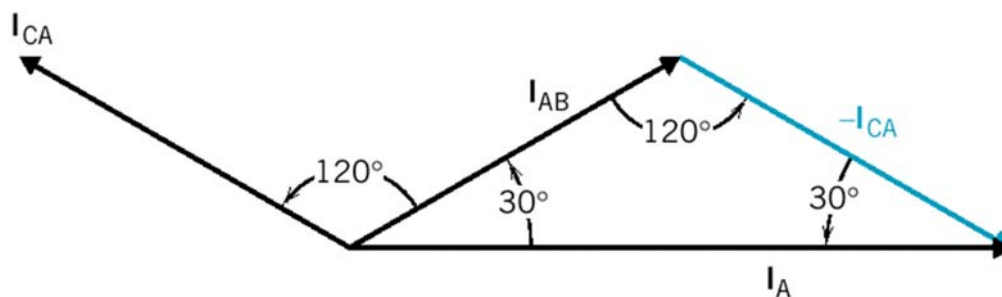

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$


$$= I \cos \phi + j \sin \phi - I \cos(\phi + 120^\circ) - j \sin(\phi + 120^\circ)$$

$$= \sqrt{3}I \angle (\phi - 30^\circ)$$

or

$$|\mathbf{I}_{aA}| = \sqrt{3} |I| \Rightarrow I_L = \sqrt{3} I_p$$

Example 12.6-1 $I_P = ?$ $I_L = ?$

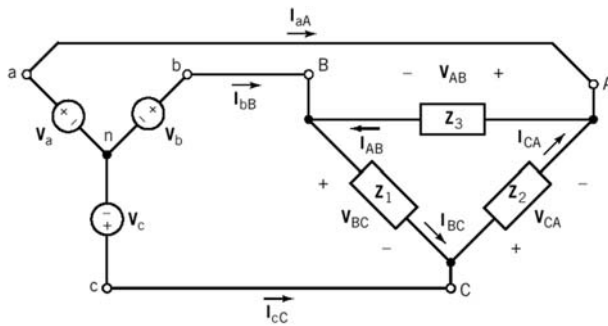

$$\mathbf{V}_a = \frac{220}{\sqrt{3}} \angle -30^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_b = \frac{220}{\sqrt{3}} \angle -150^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_c = \frac{220}{\sqrt{3}} \angle 90^\circ \quad \mathbf{V}_{\text{rms}}$$

The Δ -connected load is balanced with $\mathbf{Z}_\Delta = 10 \angle 50^\circ$

$$\mathbf{V}_{AB} = \mathbf{V}_a - \mathbf{V}_b = 220 \angle 0^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_{BC} = \mathbf{V}_b - \mathbf{V}_c = 220 \angle -120^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{V}_{CA} = \mathbf{V}_c - \mathbf{V}_a = 220 \angle -240^\circ \quad \mathbf{V}_{\text{rms}}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} = 22 \angle 50^\circ \quad \mathbf{A}_{\text{rms}}$$


$$\Rightarrow \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta} = 22 \angle -70^\circ \quad \mathbf{A}_{\text{rms}}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta} = 22 \angle -190^\circ \quad \mathbf{A}_{\text{rms}}$$


The line currents are

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA} = 22\sqrt{3} \angle 20^\circ, \mathbf{I}_{bB} = 22\sqrt{3} \angle -100^\circ, \mathbf{I}_{cC} = 22\sqrt{3} \angle -220^\circ$$

The Balanced Three-Phase Circuits

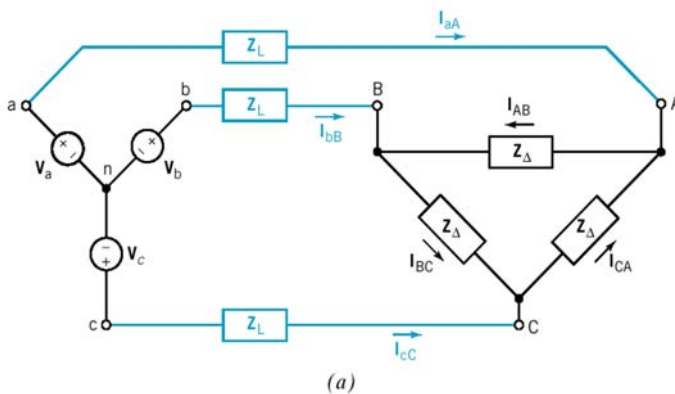


Y-to- Δ circuit

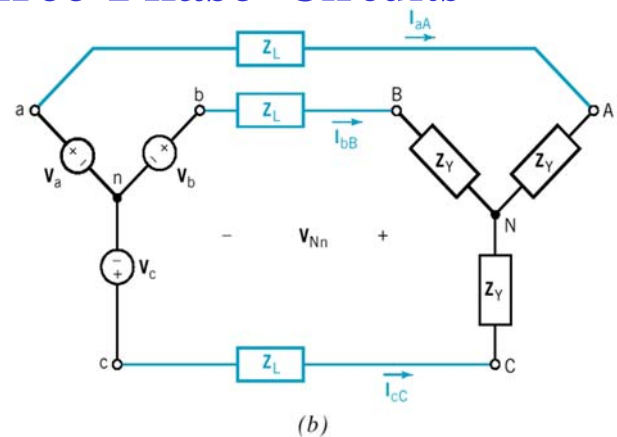

equivalent Y-to-Y circuit
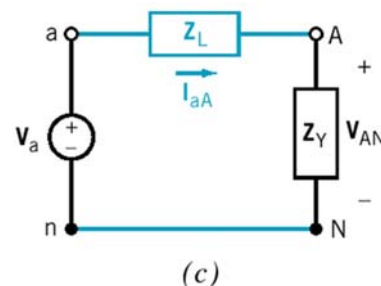
$$\mathbf{Z}_Y = \frac{\mathbf{Z}_\Delta}{3}$$



per-phase equivalent circuit

Example 12.7-1 $I_P = ?$


$$\mathbf{V}_a = 110\angle 0^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{V}_b = 110\angle -120^\circ \text{ V}_{\text{rms}}$$


$$\mathbf{V}_c = 110\angle 120^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{Z}_L = 10 + j5 \ \Omega$$

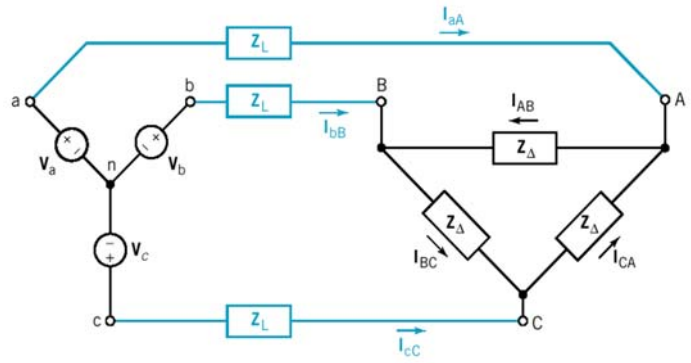
$$\mathbf{Z}_\Delta = 75 + j225 \ \Omega$$


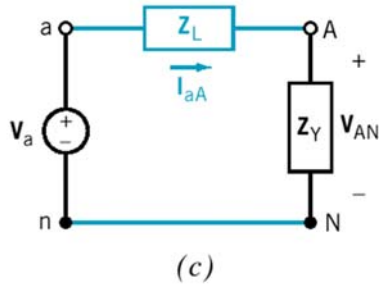
$$\mathbf{Z}_Y = \frac{\mathbf{Z}_\Delta}{3} = 25 + j75 \ \Omega$$



$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_L + \mathbf{Z}_Y} = 1.26\angle -66^\circ \text{ A}_{\text{rms}}$$

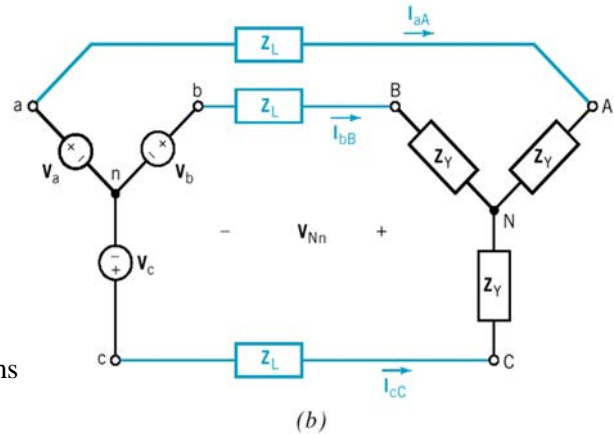

Example 12.7-1 (cont.)

$$\mathbf{I}_{bB} = 1.26\angle -186^\circ \text{ A}_{\text{rms}} \quad \text{and} \quad \mathbf{I}_{cC} = 1.26\angle -54^\circ \text{ A}_{\text{rms}}$$

The voltages in the per-phase equivalent circuit are

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} \mathbf{Z}_Y = 99.6\angle 5^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{V}_{BN} = 99.6\angle -115^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{V}_{CN} = 99.6\angle 125^\circ \text{ V}_{\text{rms}}$$

The line-to-line voltages are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} = 0.727\angle -36^\circ \text{ A}_{\text{rms}}$$

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} = 172\angle 35^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{V}_{BC} = \mathbf{V}_{BN} - \mathbf{V}_{CN} = 172\angle -85^\circ \text{ V}_{\text{rms}}$$

$$\mathbf{V}_{CA} = \mathbf{V}_{CN} - \mathbf{V}_{AN} = 172\angle 155^\circ \text{ V}_{\text{rms}}$$

$$\Rightarrow \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta} = 0.727\angle -156^\circ \text{ A}_{\text{rms}}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta} = 0.727\angle 84^\circ \text{ A}_{\text{rms}}$$

Instantaneous and Average Power in BTP Circuits

One advantage of three-phase power is the smooth flow of energy to the load.

The instantaneous power

$$v_{ab} = V \cos \omega t, v_{bc} = V \cos(\omega t - 120^\circ),$$

$$\text{and } v_{ca} = V \cos(\omega t - 240^\circ)$$

$$p(t) = \frac{v_{ab}^2}{R} + \frac{v_{bc}^2}{R} + \frac{v_{ca}^2}{R}$$

$$\cos^2 \omega t = \frac{(1 + \cos 2\omega t)}{2}$$

$$= \frac{V^2}{2R} [1 + \cos 2\omega t + 1 + \cos 2(\omega t - 120^\circ) + 1 + \cos 2(\omega t - 240^\circ)]$$


$$= \frac{3V^2}{2R} + \frac{V^2}{2R} \underbrace{[\cos 2\omega t + \cos(2\omega t - 240^\circ) \cos(2\omega t - 480^\circ)]}_{0}$$

$$= \frac{3V^2}{2R}$$

Instantaneous and Average Power in BTP Circuits

The total average power delivered to the balanced Y-connected load is

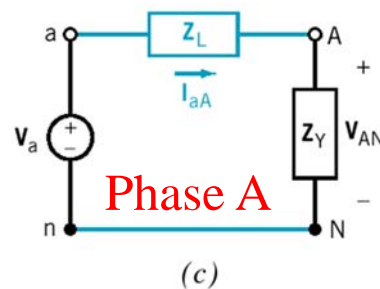
$$\mathbf{I}_{aA} = I_L \angle \theta_{AI}, \mathbf{V}_{AN} = V_P \angle \theta_{AV}$$



$$\begin{aligned} P_Y &= 3P_A = 3V_P I_L \cos(\theta_{AV} - \theta_{AI}) \\ &= 3V_P I_L \cos(\theta) \\ &= 3 \frac{V_L}{\sqrt{3}} I_L \cos(\theta) \\ &= \sqrt{3} V_L I_L \cos(\theta) \end{aligned}$$

Instantaneous and Average Power in BTP Circuits

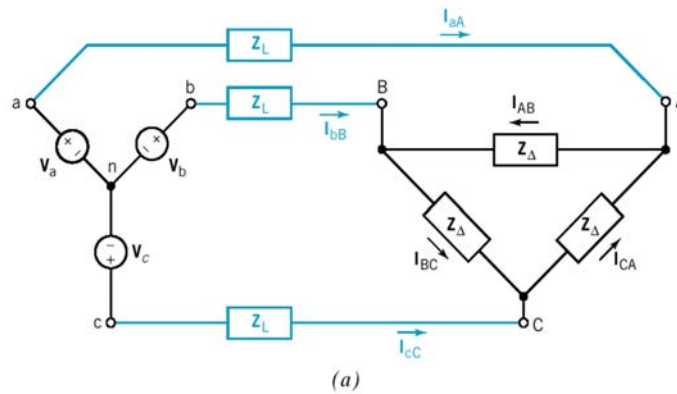
The total average power delivered to the balanced Δ -connected load is



$$\begin{aligned}
 P_{\Delta} &= 3P_{AB} = 3V_{AB}I_{AB}\cos(\theta) \\
 &= 3(\sqrt{3}V_P)\frac{I_L}{\sqrt{3}}\cos(\theta) \\
 &= 3V_P I_L \cos(\theta)
 \end{aligned}$$

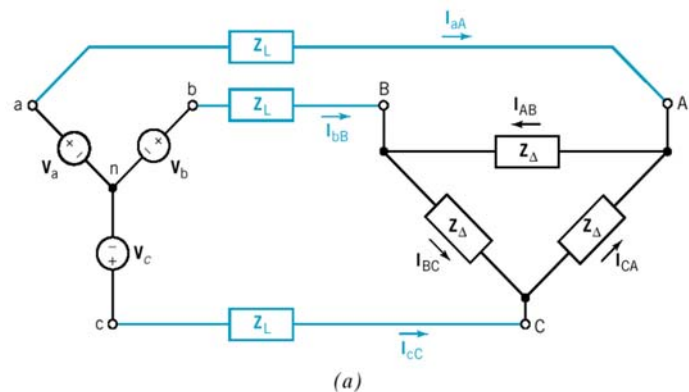Example 12.8-1 $P = ?$

$$\begin{aligned}
 \mathbf{V}_a &= 110\angle 0^\circ \quad \mathbf{V}_{\text{rms}} \\
 \mathbf{V}_b &= 110\angle -120^\circ \quad \mathbf{V}_{\text{rms}} \\
 \mathbf{V}_c &= 110\angle 120^\circ \quad \mathbf{V}_{\text{rms}} \\
 \mathbf{Z}_L &= 10 + j5 \quad \Omega \\
 \mathbf{Z}_{\Delta} &= 75 + j225 \quad \Omega
 \end{aligned}$$




$$\mathbf{I}_{aA} = \frac{\mathbf{V}_a}{\mathbf{Z}_L + \mathbf{Z}_Y} = 1.26\angle -66^\circ \text{ A}_{\text{rms}}$$

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} \mathbf{Z}_Y = 99.6\angle 5^\circ \text{ V}_{\text{rms}}$$

$$P = 3(99.6)(1.26)\cos(5^\circ - (-66^\circ)) = 122.6 \text{ W}$$

Two-Wattmeter Power Measurement

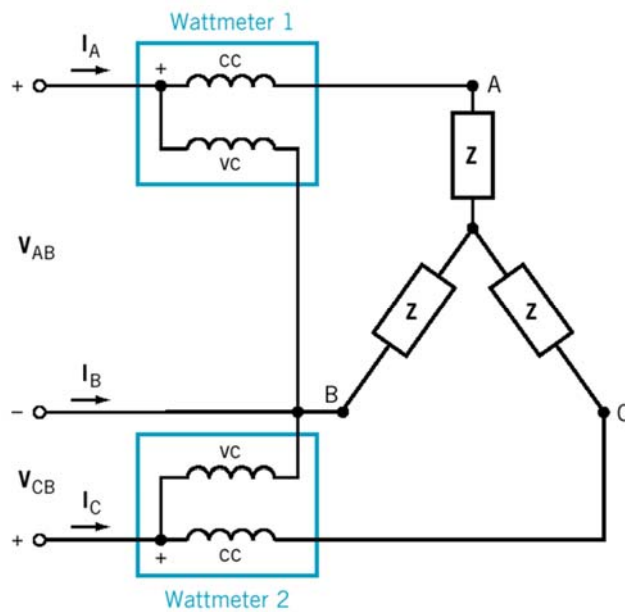

cc = current coil
vc = voltage coil

W1 read

$$P_1 = V_{AB} I_A \cos \theta_1$$

W2 read

$$P_2 = V_{CB} I_C \cos \theta_2$$

For balanced load with *abc* phase sequence

$$\theta_1 = \theta_a + 30^\circ \quad \text{and} \quad \theta_2 = \theta_a - 30^\circ$$

θ_a is the angle between phase current and phase voltage of phase *a*

Two-Wattmeter Power Measurement(cont.)

$$\begin{aligned} P &= P_1 + P_2 \\ &= 2V_L I_L \cos \theta \cos 30^\circ \\ &= \sqrt{3} V_L I_L \cos \theta \end{aligned}$$

To determine the power factor angle

$$P_1 + P_2 = V_L I_L 2 \cos \theta \cos 30^\circ$$

$$P_1 - P_2 = V_L I_L (-2 \sin \theta \sin 30^\circ)$$

$$\frac{P_1 + P_2}{P_1 - P_2} = \frac{V_L I_L 2 \cos \theta \cos 30^\circ}{V_L I_L (-2 \sin \theta \sin 30^\circ)} = \frac{-\sqrt{3}}{\tan \theta}$$

$$\therefore \tan \theta = \sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \quad \text{or} \quad \theta = \tan^{-1} \left(\sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \right)$$

Example 12.9-1 $P = ?$

$$\mathbf{Z} = 10\angle 45^\circ$$

line-to-line voltage = 220Vrms


The phase voltage

$$\mathbf{V}_A = \frac{220}{\sqrt{3}} \angle -30^\circ$$


The line current

$$\mathbf{I}_A = \frac{\mathbf{V}_A}{\mathbf{Z}} = \frac{220\angle -30^\circ}{10\sqrt{3}\angle 45^\circ} = 12.7\angle -75^\circ \text{ and } \mathbf{I}_B = 12.7\angle -195^\circ$$
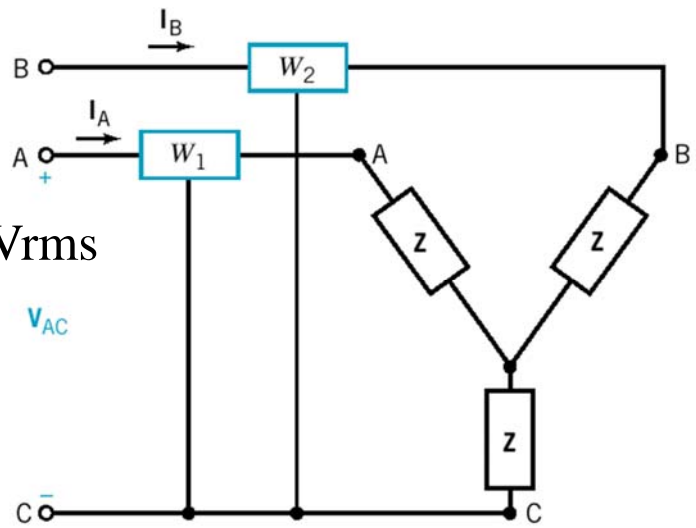
$$P_1 = V_{AC} I_A \cos \theta_1 = 2698 \text{ W} \quad \Rightarrow \quad P = P_1 + P_2 = 3421 \text{ W}$$
$$P_2 = V_{BC} I_B \cos \theta_2 = 723 \text{ W}$$



Electrodynamic Wattmeter

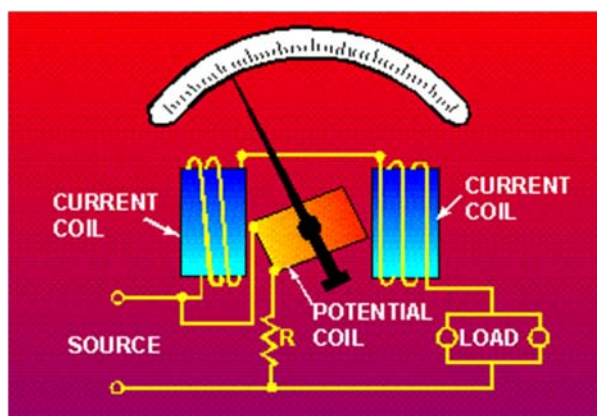



Digital Power Meter



VAR Meter



***pf* Meter**

Summary

- ✚ Three-Phase voltages
- ✚ The Y-to-Y Circuits
- ✚ The Δ -Connected Source and Load
- ✚ The Y-to- Δ Circuits
- ✚ Balanced Three-Phase Circuits
- ✚ Instantaneous and Average Power in Bal. 3- ϕ Load
- ✚ Two-Wattmeter Power Measurement