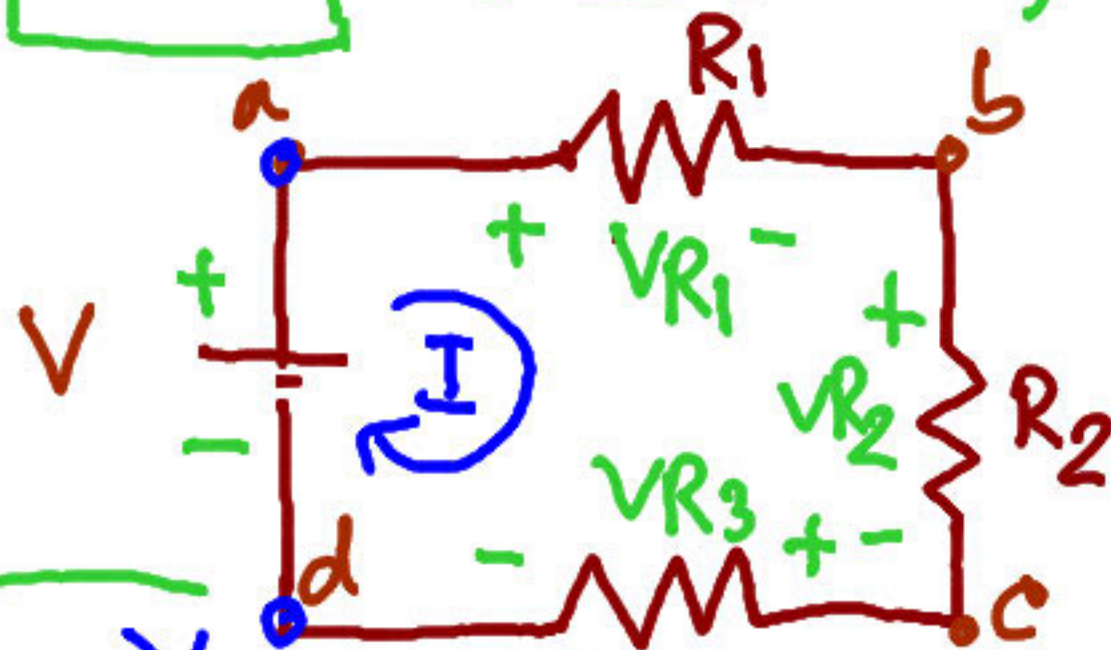


Kirchoff's Law

- Kirchoff's Voltage Law (KVL)
- Kirchoff's Current Law (KCL)

□ KVL ($\sum v = 0$)



→ Loop $\Rightarrow a-b-c-d-a$




$$V_{R1} + V_{R2} + V_{R3} - V = 0$$

$$IR_1 + IR_2 + IR_3 = V$$

$$I(R_1 + R_2 + R_3) = V$$

$$I = \frac{V}{R_1 + R_2 + R_3} \quad \leftarrow \text{Ohm's Law}$$

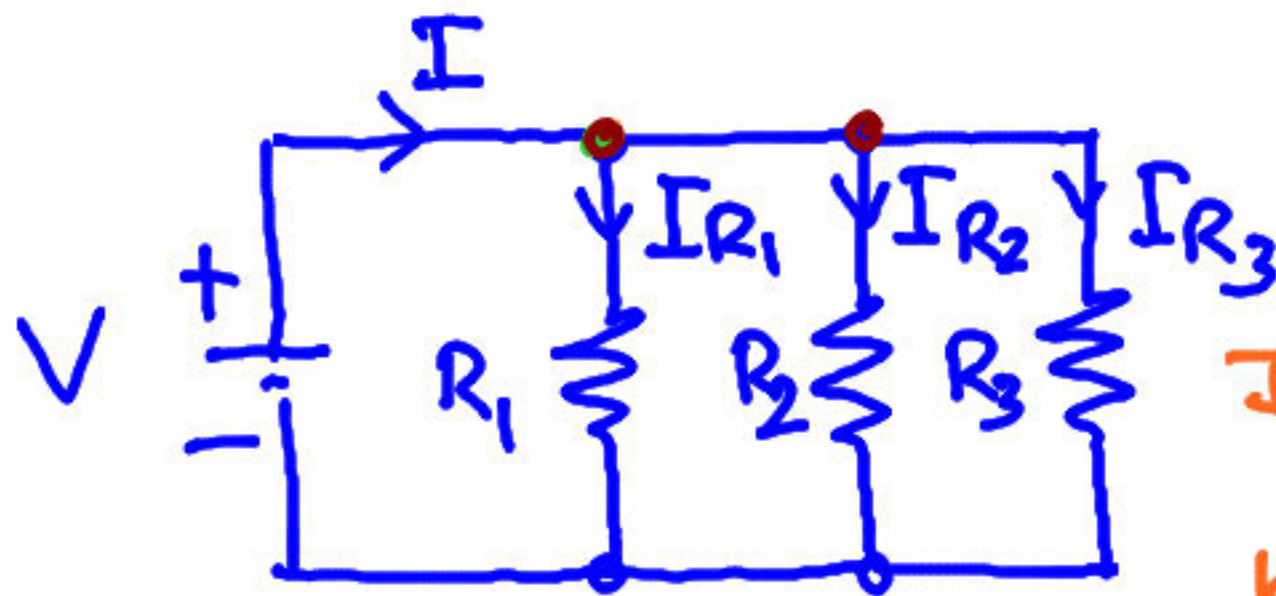□ **KCL** ($\sum I = 0$) กฎ: หัดในหัดเข้า = หัด: หัดในหัดออก



$\Rightarrow I_{R_1} + I_{R_2} + I_{R_3} - I = 0$

KCL $\frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = I$

$$V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = I$$

$\Rightarrow$
Ohm's Law

$V \left(\frac{1}{R_T} \right) = I$

Cramer's Rule

Cramer's Rule (120) (-20) អនុវត្តចំពោះ ២ ចំណុចប្រឈម

Ex 1 $\begin{matrix} (120) & (-20) \\ 6x + 4y & = 20 \end{matrix}$ — ① จงหา x, y

$$10x + 12y = 30 \quad - (2)$$

$$\begin{matrix} \text{J.V.S} & & \text{ตัวแปร} \\ \begin{bmatrix} 6 & 4 \\ 10 & 12 \end{bmatrix} \times \begin{bmatrix} x \\ y \end{bmatrix} & = & \begin{bmatrix} 20 \\ 30 \end{bmatrix} \end{matrix}$$

$$\begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 20 \\ 30 \end{bmatrix} \begin{bmatrix} 6 & 4 \\ 10 & 12 \end{bmatrix}^{-1}$$

$$\begin{bmatrix} 6 & 4 \\ 10 & 12 \end{bmatrix}^{-1}$$

$$D = \begin{bmatrix} 6 & 4 \\ 10 & 12 \end{bmatrix} = 72 - 40 = 32$$

x

$$x = \frac{\begin{bmatrix} 20 \\ 30 \end{bmatrix} \begin{bmatrix} 4 \\ 12 \end{bmatrix}}{D} = \frac{(20)(12) - (30)(4)}{32} = 120$$

$$y = \begin{bmatrix} 6 & 20 \\ 10 & 30 \end{bmatrix} / D = \frac{(6)(30) - (10)(20)}{32} = -20$$

Ex 2 จงหาค่า I_1, I_2 และ I_3

$$10I_1 - 2I_2 - 4I_3 = 10$$

$$-2I_1 + 12I_2 - 6I_3 = -34$$

$$-4I_1 - 6I_2 + 14I_3 = 40$$

จ.ว.จ

↓ A

↓ B

$$\begin{bmatrix} 10 & -2 & -4 \\ -2 & 12 & -6 \\ -4 & -6 & 14 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -34 \\ 40 \end{bmatrix}$$

$[I] = [A]^{-1} [B] =$

$$D = \begin{bmatrix} 10 & -2 & -4 \\ -2 & 12 & -6 \\ -4 & -6 & 10 \end{bmatrix}$$

$\rightarrow 192 \rightarrow 360 \rightarrow 56$
 $\rightarrow 1680 \rightarrow -48 \rightarrow -48$

$$= 1680 - 48 - 48 - (192 + 360 + 56) = 976$$

$$\therefore I_1 = \frac{\begin{vmatrix} 10 & -2 & -4 & 10 & -2 \\ -34 & 12 & -6 & -34 & 12 \\ 40 & -6 & 10 & 40 & -6 \end{vmatrix}}{976}$$


$$= \frac{1952}{976} = 2 \text{ A}$$

$$I_2 = -1 \text{ A}, \quad I_3 = 3 \text{ A}$$

Loop Analysis

$$(KVL) \Rightarrow \sum V = 0$$

①

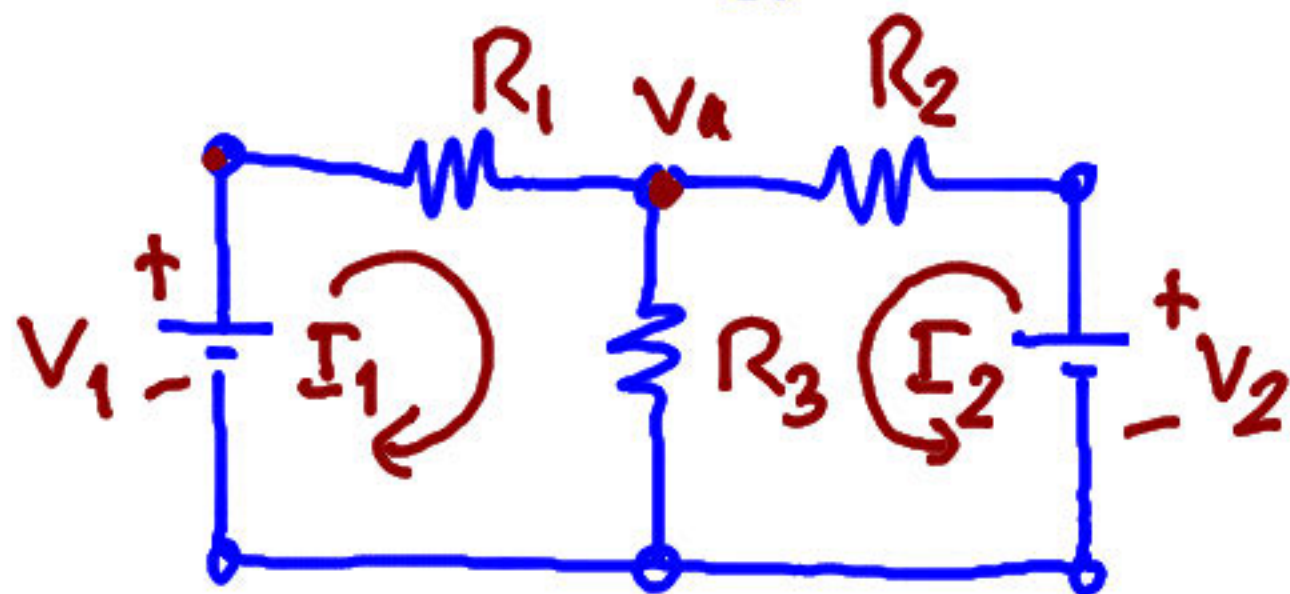

KVL

Loop #1

$$I_1 R_1 + I_1 R_3 + \underline{I_2 R_3} = V_1$$


$$I_1 (R_1 + R_3) + \underline{I_2 R_3} = V_1$$

Loop #2

$$I_1 R_3 + \underline{I_2 R_2} + \underline{I_2 R_3} = V_2$$

$$I_1 R_3 + I_2 (R_2 + R_3) = V_2$$

②

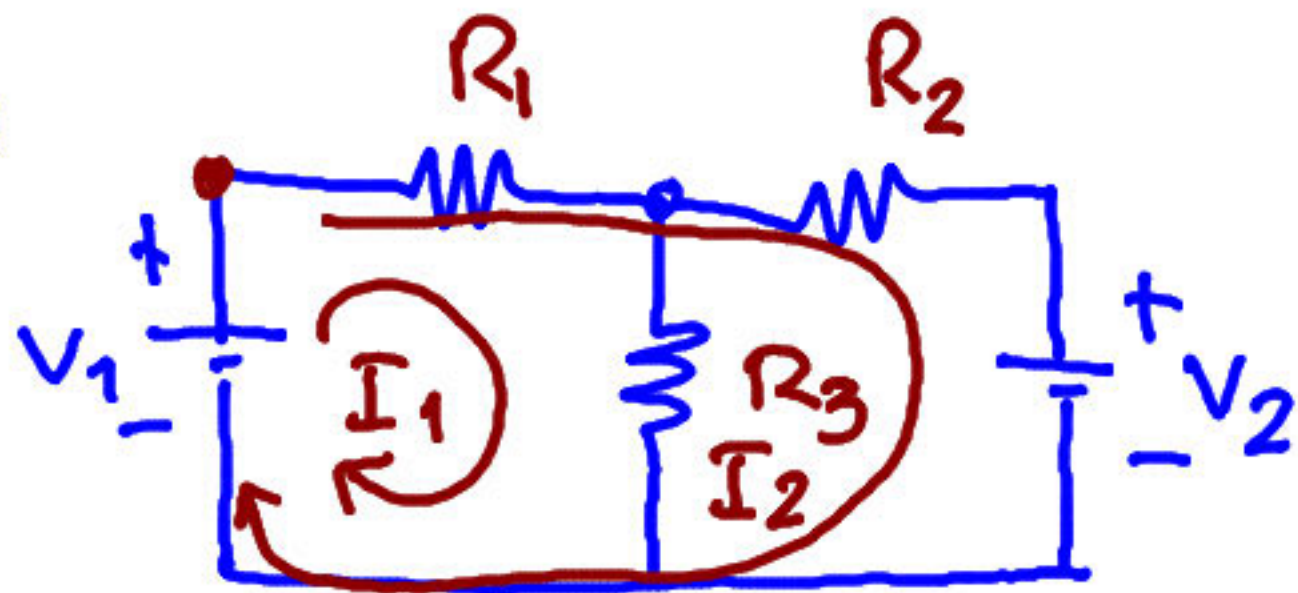

Loop #1

$$I_1 R_1 + I_1 R_3 + I_2 R_1 = V_1$$

$$I_1 (R_1 + R_3) + I_2 R_1 = V_1$$

Loop #2


$$I_1 R_1 + I_2 R_1 + I_2 R_2 = V_1 - V_2$$

$$I_1 R_1 + I_2 (R_1 + R_2) = V_1 - V_2$$

$$V_1 - V_2 = V_1 - V_2$$

$$V_1 + V_2 = V_1 + V_2$$

Ex 3

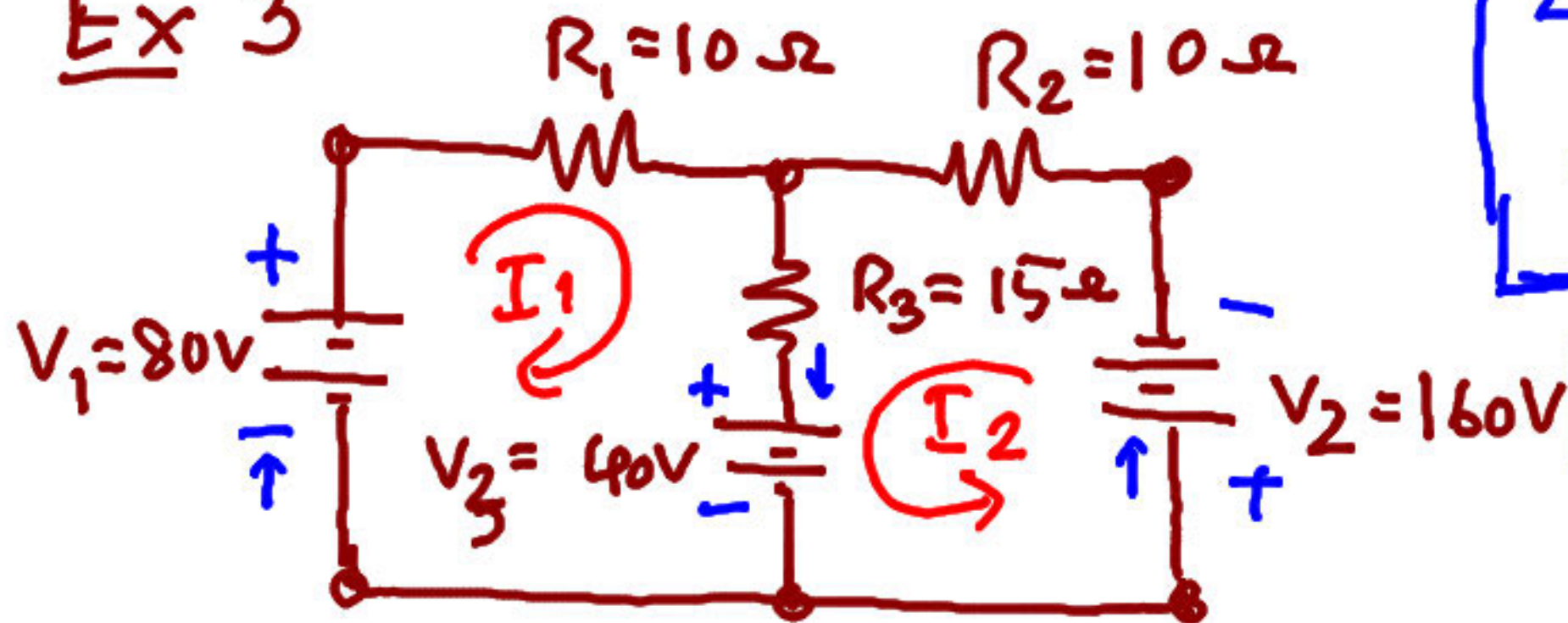

$$25I_1 + 15I_2 = 40$$

$$5I_1 + 3I_2 = 8 \quad \text{--- (1)}$$

Loop #2

$$I_1 R_3 + I_2 R_2 + I_2 R_3 + V_2 + V_3 = 0$$

จากกฎของ Kirchhoff ในลูปผ่านตัวต้านทานทุกตัว

→ สมมติการไหลของกระแสในลูป

→ Loop #1 $\Rightarrow I_1 R_1 + I_1 R_3 + I_2 R_3 - V_1 + V_3 = 0$

$$I_1 (R_1 + R_3) + I_2 R_3 = V_1 - V_3$$

$$I_1 (25) + I_2 (15) = 80 - 40$$

$$I_1 R_3 + I_2 (R_2 + R_3) = -V_2 - V_3$$

$$15I_1 + 25I_2 = -200$$

545000

$$3I_1 + 5I_2 = -40 \quad \text{--- (2)}$$

$$5I_1 + 3I_2 = 8 \quad \text{--- (1)}$$

แก้สมการ 2 ตัวแปร หา I_1, I_2

$$\begin{bmatrix} 5 & 3 \\ 3 & 5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 8 \\ -40 \end{bmatrix}$$

$$I_1 = \frac{\begin{bmatrix} 8 & 3 \\ -40 & 5 \end{bmatrix}}{16}$$


$$= \frac{40 - (-120)}{16} = \frac{160}{16} = 10 \text{ A}$$

$$I_2 = \frac{\begin{bmatrix} 5 & 8 \\ 3 & -40 \end{bmatrix}}{16}$$

$$= \frac{-200 - 24}{16} = -14 \text{ A}$$

I_2 ติดลบ แปลว่า
ว่า เราสมมติ
ทิศทาง I_2 ผิด

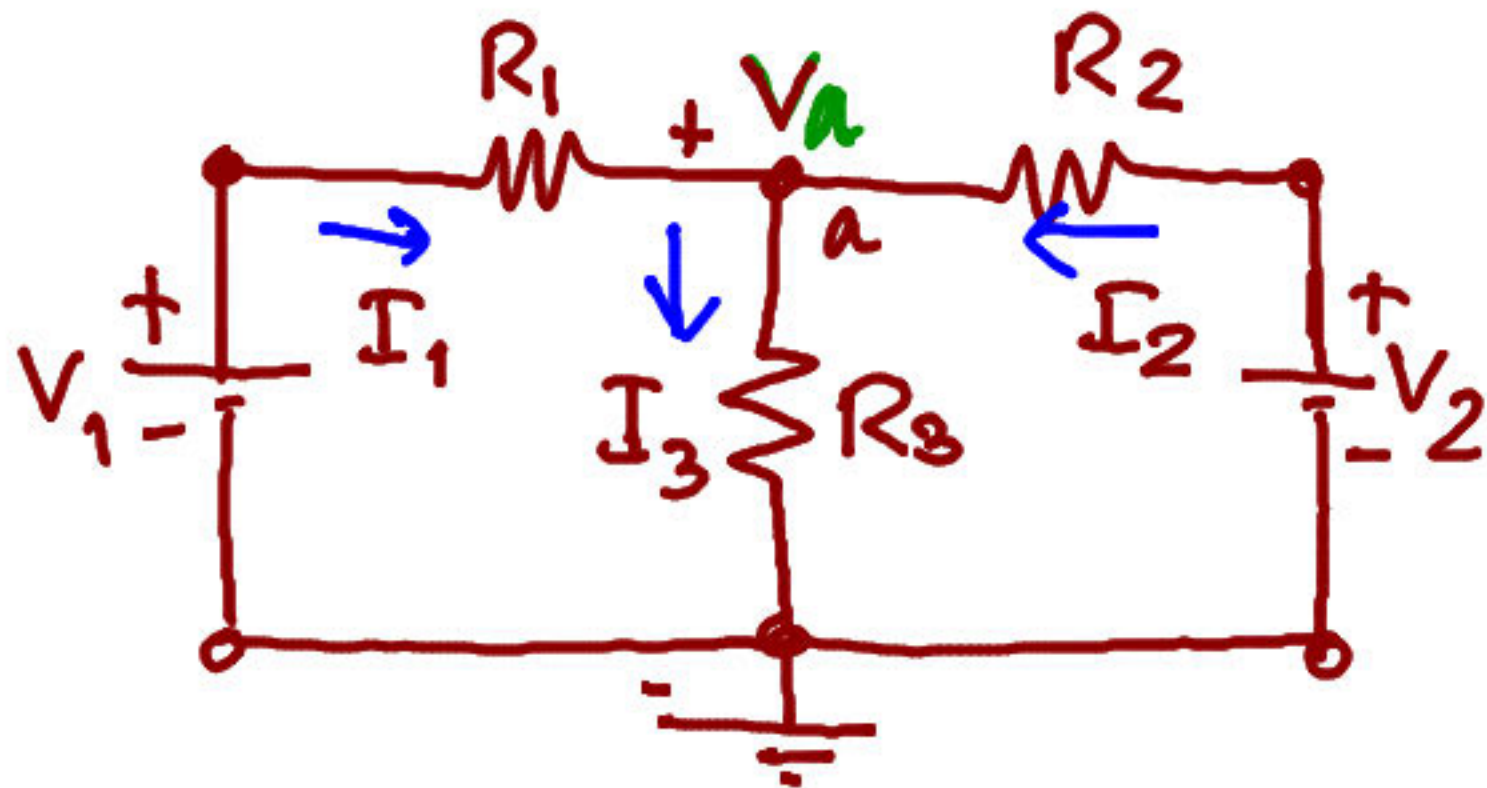□ Node Analysis (KCL) $\Rightarrow \sum I = 0$




Node V_a ($\sum I = 0$)
 $\text{KCL} \quad \textcircled{I_1 + I_2 - I_3 = 0}$

$$\frac{V_1}{R_1} - \frac{V_a}{R_1} + \frac{V_2}{R_2} - \frac{V_a}{R_2} - \frac{V_a}{R_3} = 0$$

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} - \frac{V_a}{R_3} = 0$$
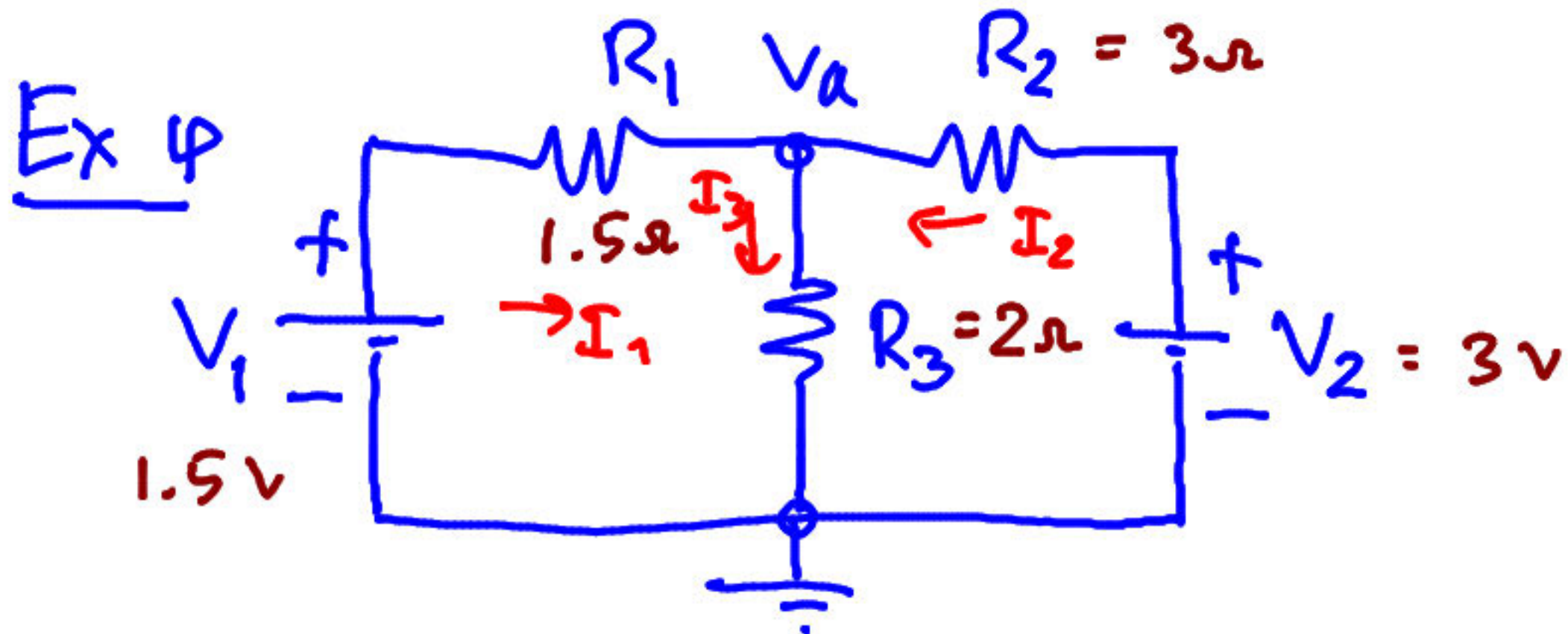
$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_a}{R_1} + \frac{V_a}{R_2} + \frac{V_a}{R_3}$$



ให้ $V_1 = 1.5V$, $V_2 = 3V$, $R_1 = 1.5\Omega$, $R_2 = 3\Omega$, $R_3 = 2\Omega$

หาค่า I_1 , I_2 และ I_3

วิธีทำ

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_a}{R_1} + \frac{V_a}{R_2} + \frac{V_a}{R_3}$$

$$\frac{1.5}{1.5} + \frac{3}{3} = \frac{V_a}{1.5} + \frac{V_a}{3} + \frac{V_a}{2}$$

$$2 = \left[\frac{4+2+3}{6} \right] V_a \quad \left| \begin{array}{l} V_{R_1} = V_1 - V_a \\ V_{R_2} = V_2 - V_a \\ V_{R_3} = V_a \end{array} \right.$$

$$2 = \frac{9}{6} V_a$$


$$V_a = \frac{12}{9} = 1.333 \text{ Volt}$$

$$\therefore I_1 = \frac{V_1 - V_a}{R_1} = \frac{1.5 - 1.333}{1.5} = 0.111 \text{ A}$$

$$I_2 = \frac{V_2 - V_a}{R_2} = \frac{3 - 1.333}{3} = 0.555 \text{ A}$$

$$I_3 = \frac{V_a}{R_3} = \frac{1.333}{2} = 0.666 \text{ A}$$


โจทย์ # 2

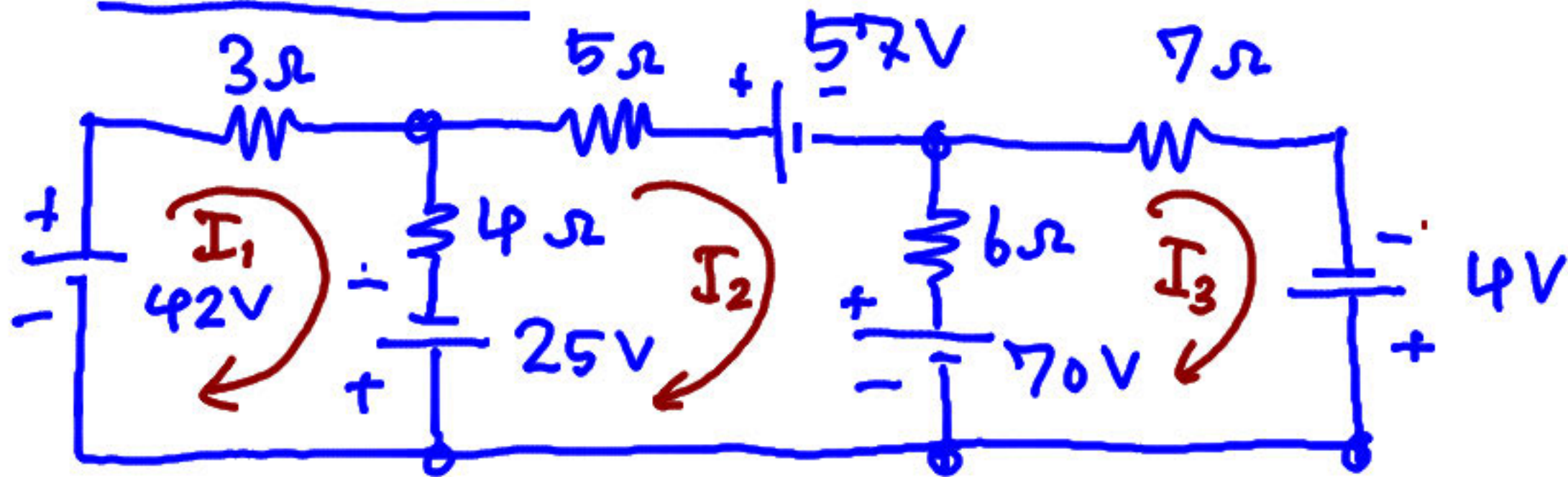

จงหาค่าของ I_1 , I_2 และ I_3


แบบฝึกหัดที่ 2

①

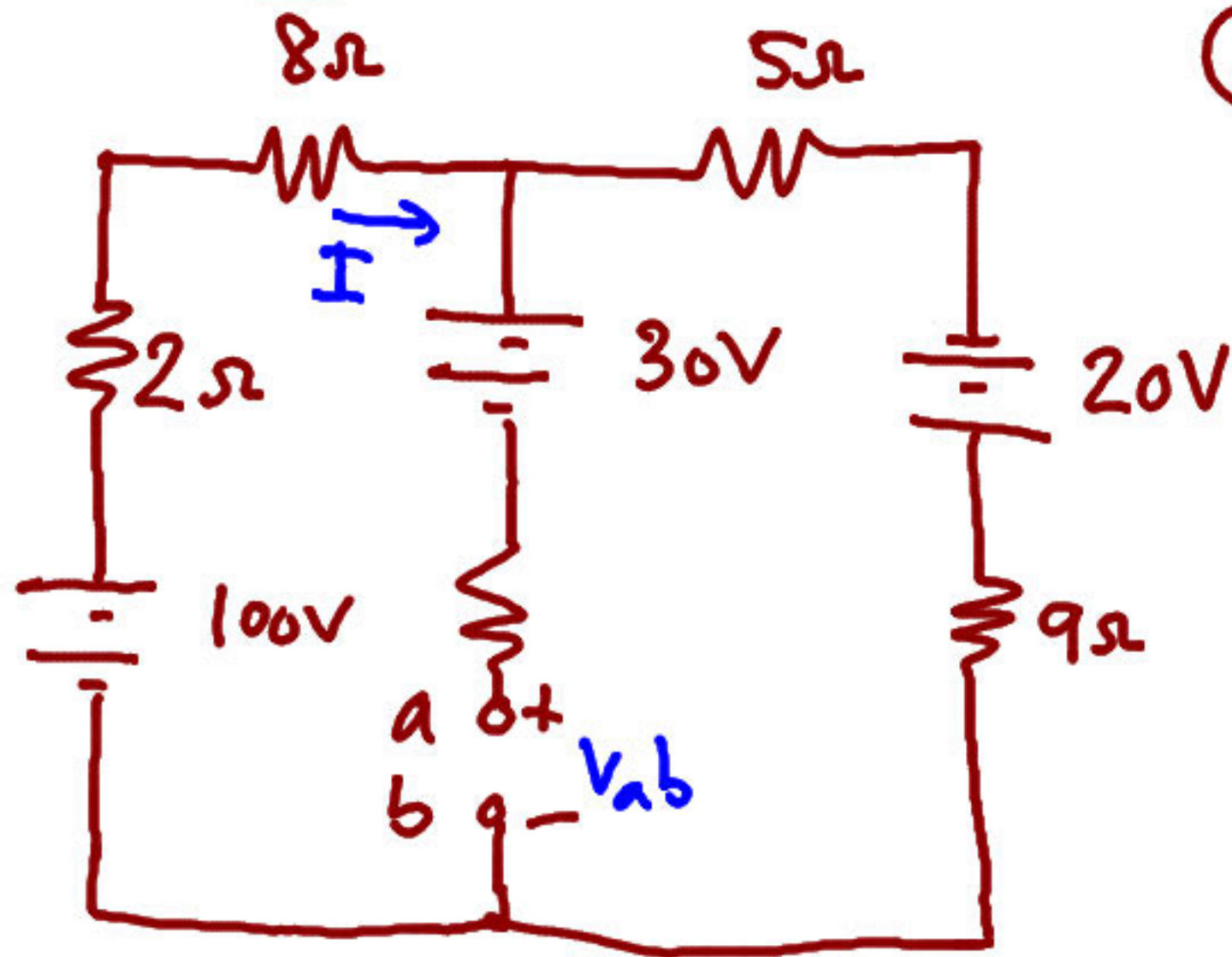


หาค่า I และ V_{ab}

②

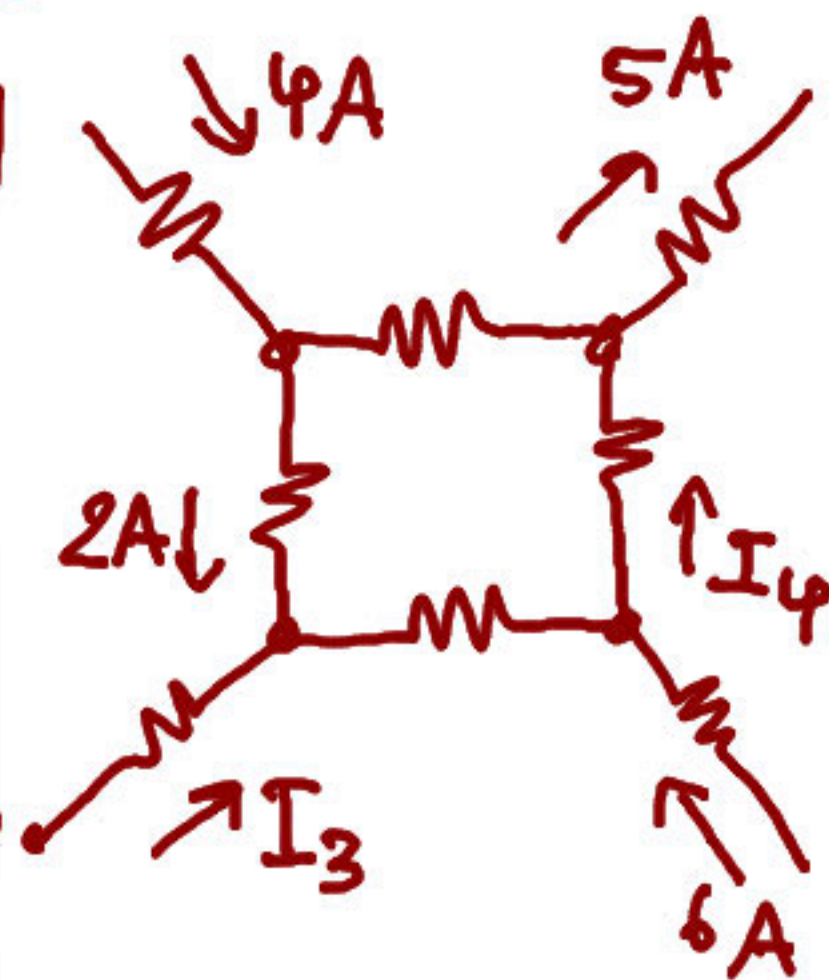


หาค่า I_3, I_4

③

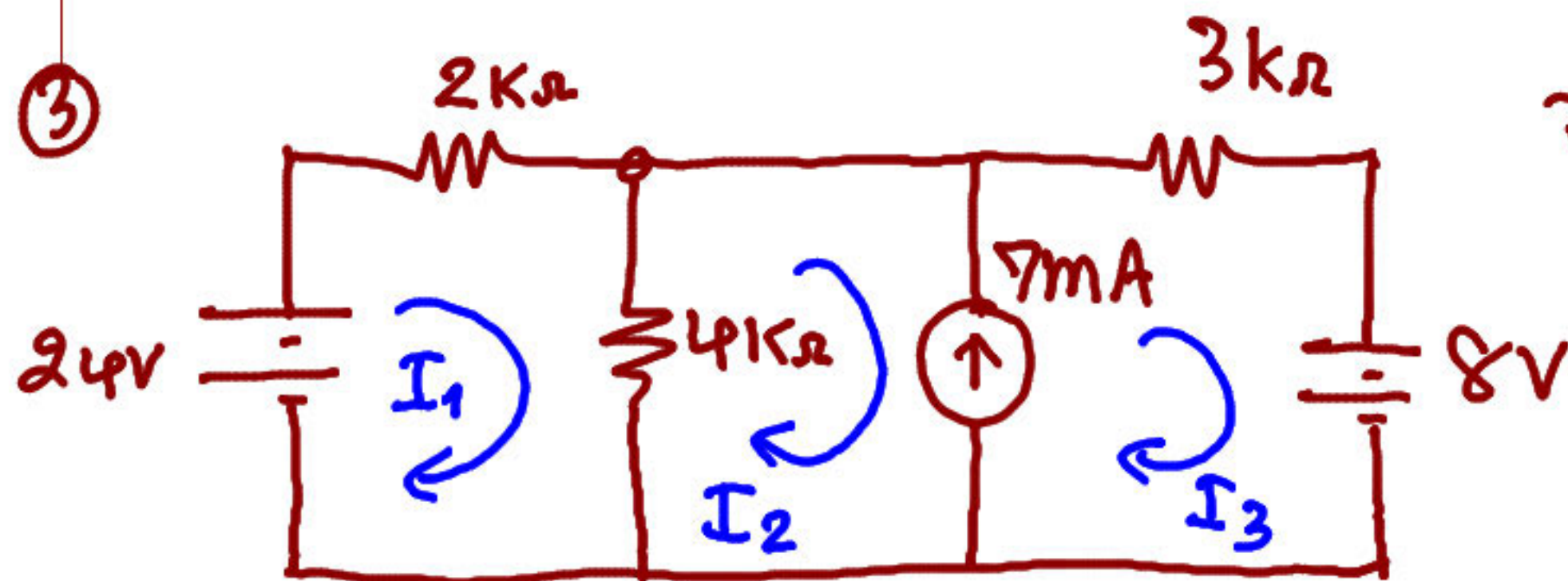

જાણ I_1, I_2, I_3

④

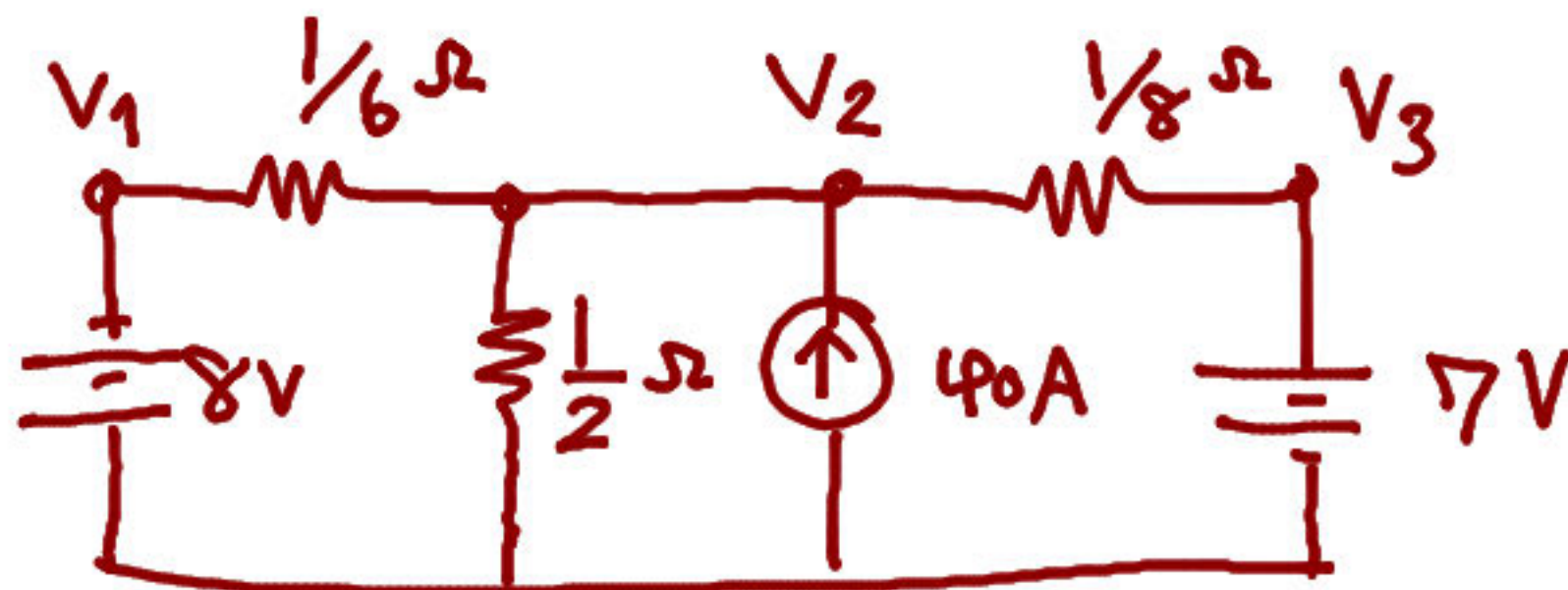

જાણ V_1, V_2 ના: V_3