

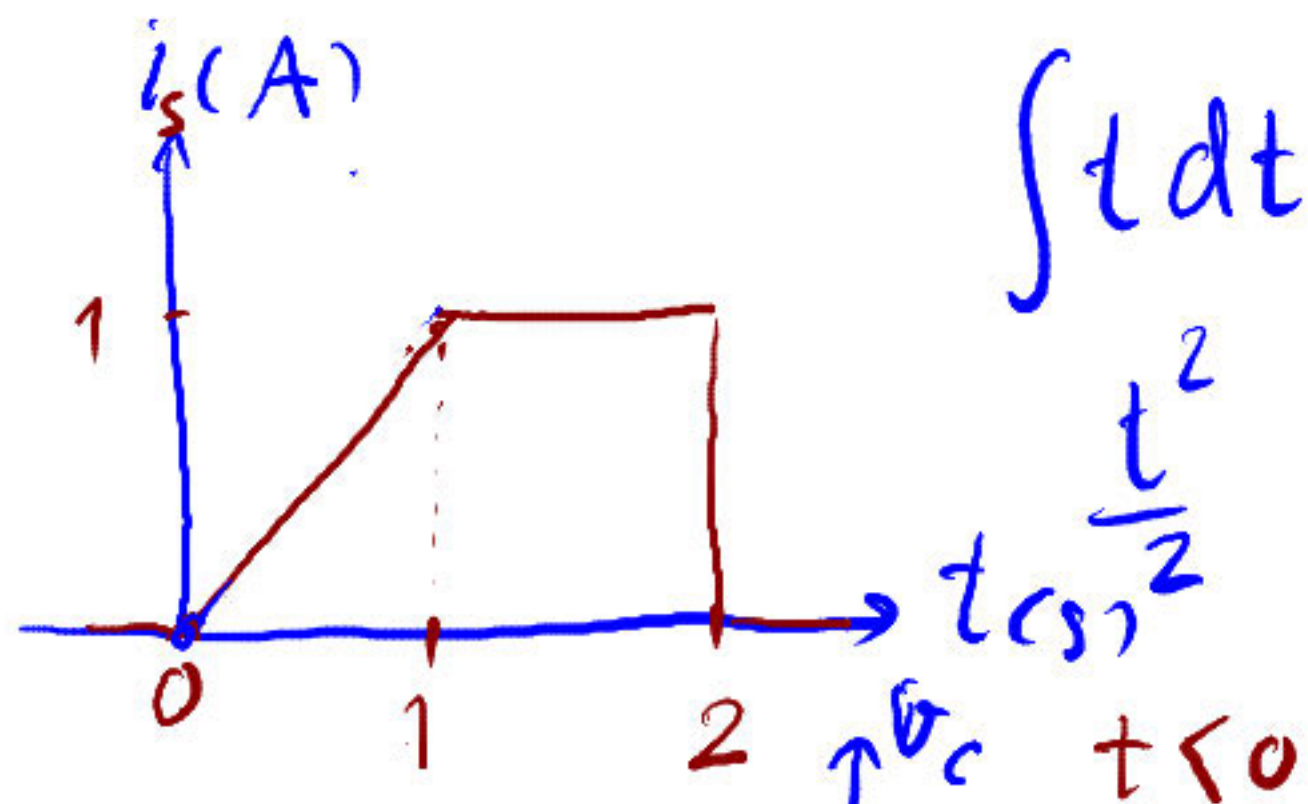


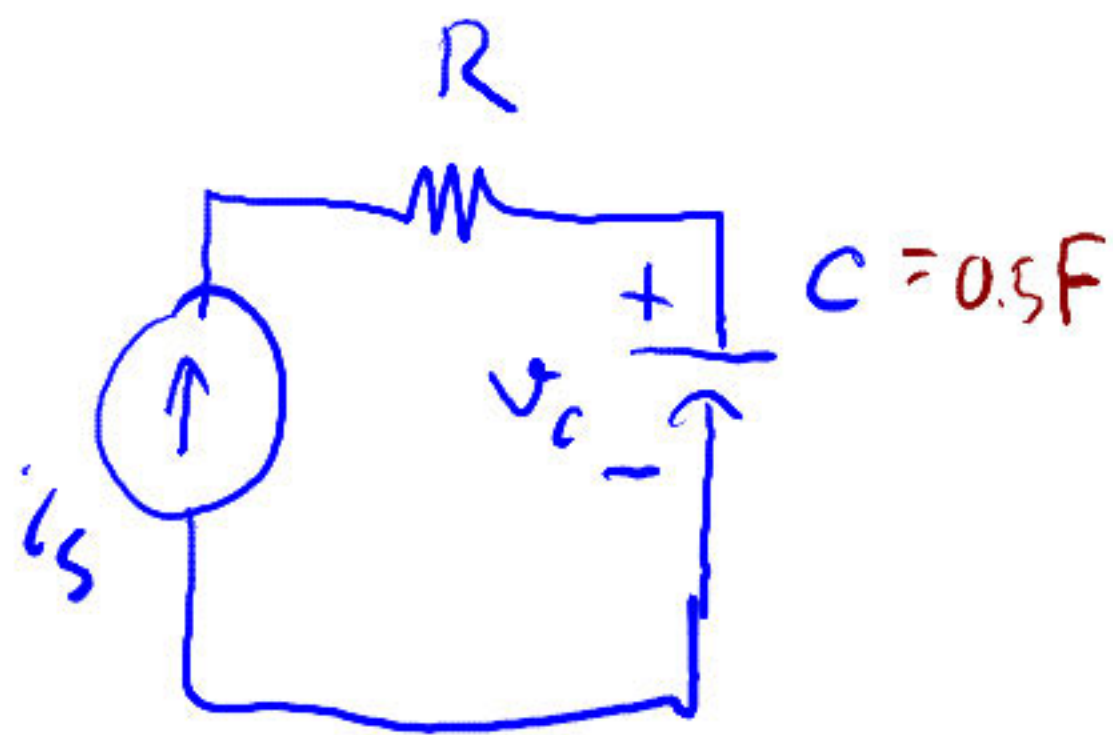
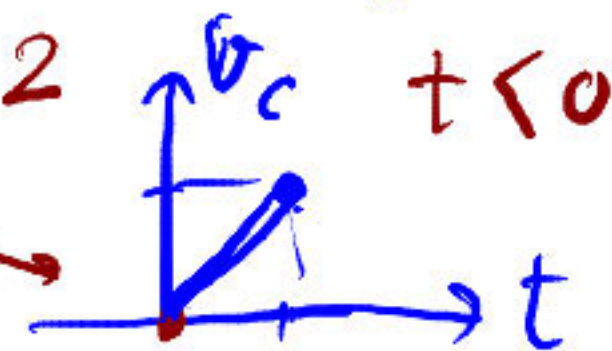
$$i = \begin{cases} 0 & ; t \leq 0 \\ t & ; 0 \leq t < 1 \\ 1 & ; 1 \leq t < 2 \\ 0 & ; t \geq 2 \end{cases}$$



$$v_c = \frac{1}{C} \int i d\tau + v(t_0)$$

$$v_c = \frac{1}{0.5} \int_0^t \tau d\tau + 0$$

$$= t^2 - 0^2 = t^2$$


①

Method of finding RL (RL + Source)


1. หา $\tau = L_{eq}/R_{eq}$ ที่ $t \geq 0$
2. หา $i_L(0^+) = i_L(0^-)$; สำหรับ $i_L(0^-)$ จงหาที่ $t < 0$
ที่ $t = 0^-$ (ถ้าเป็นแหล่งจ่าย DC, $L = \text{Short}$)
3. หา $f(0^+)$ จงหาที่ $t = 0^+$ (สำหรับ $L = i_L(0^+)$
ถ้า $i_L(0^+) = 0$ จงหาที่ $t = 0^+$)
4. หา Final Value, $f(\infty)$ จงหาที่ $t = \infty$
(ถ้าเป็น DC Source, $L = \text{Short}$)
5. $f(t) = f(\infty) + [f(0^+) - f(\infty)] e^{-t/\tau}, t > 0$

②

Ex 1 จงหา v และ i เมื่อ $t > 0$

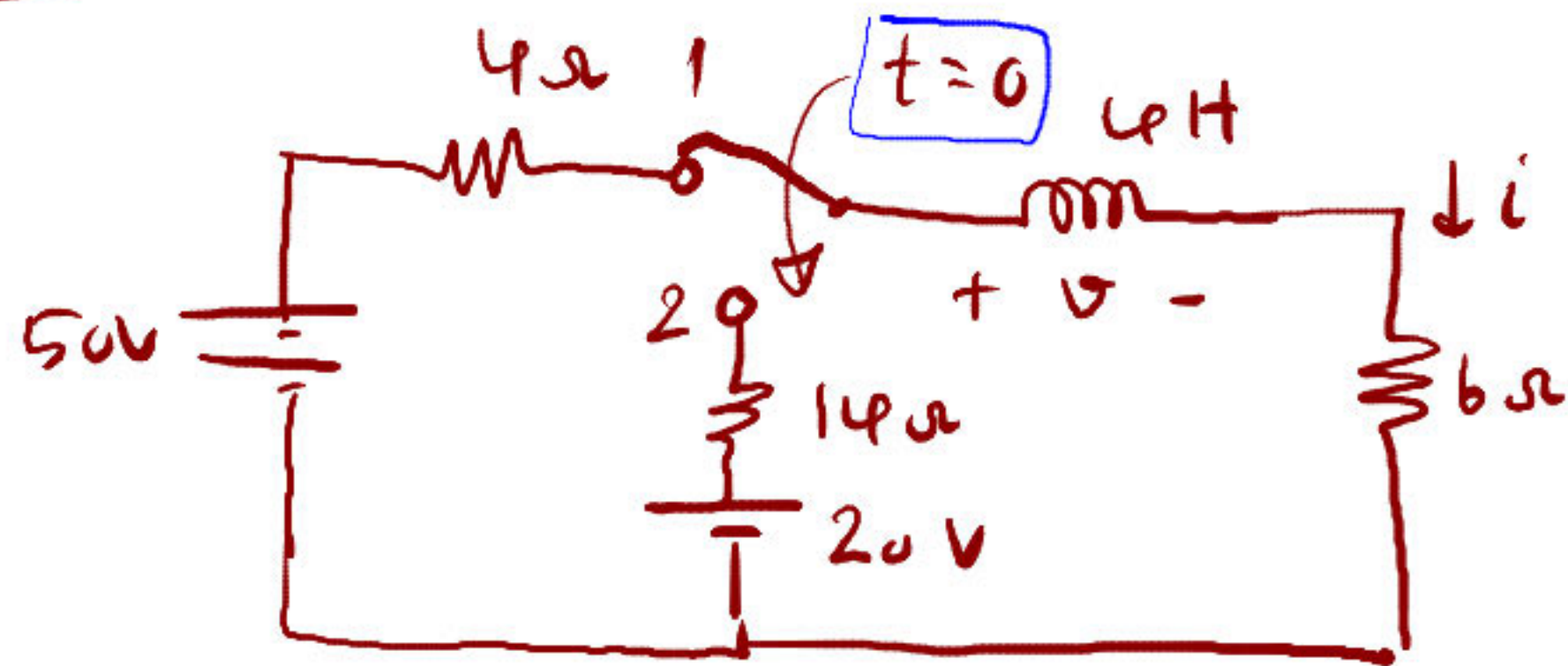

Step 1 $\tau = L/R_{eq} ; t > 0$

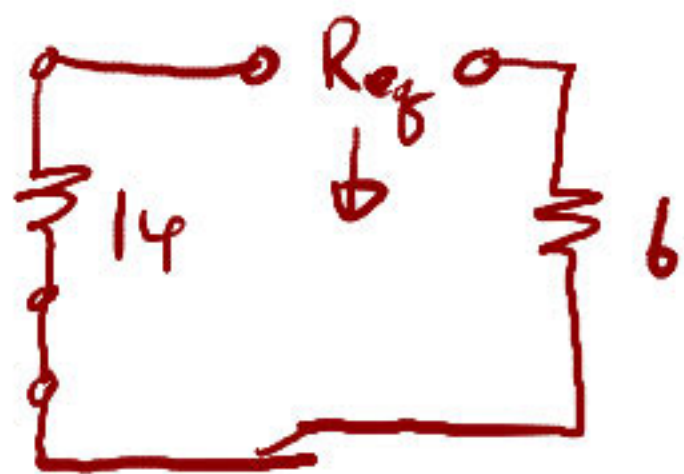


$$R_{eq} = 20$$


$$\tau = \frac{4}{20} = 0.2 \text{ s}$$

Step ② w.r. $V(0^+)$, $i(0^+)$ w. $t < 0$

$$V(0^+) \neq V(0^-), i(0^+) = i(0^-)$$

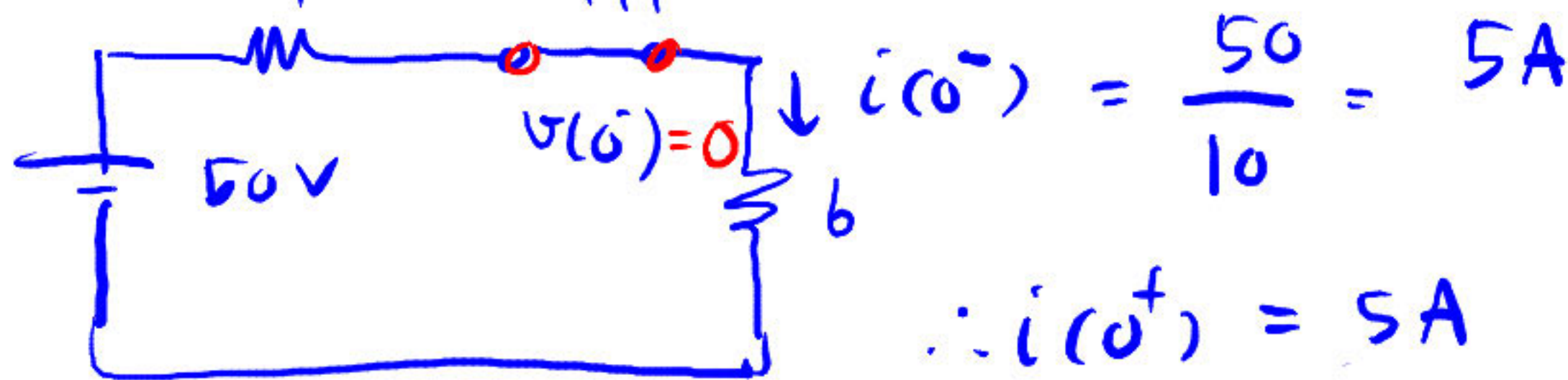

Step ③ w. $t = 0^+$ (sw = Z)

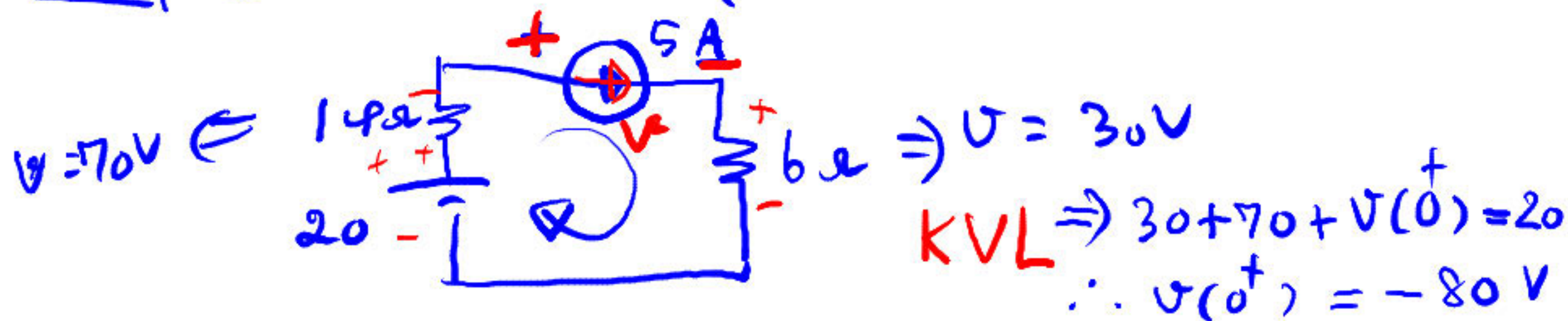


$$\frac{\tau}{0.2} = 0.5t$$

Step ④

$$t = \infty \text{ (sw = 2)}$$
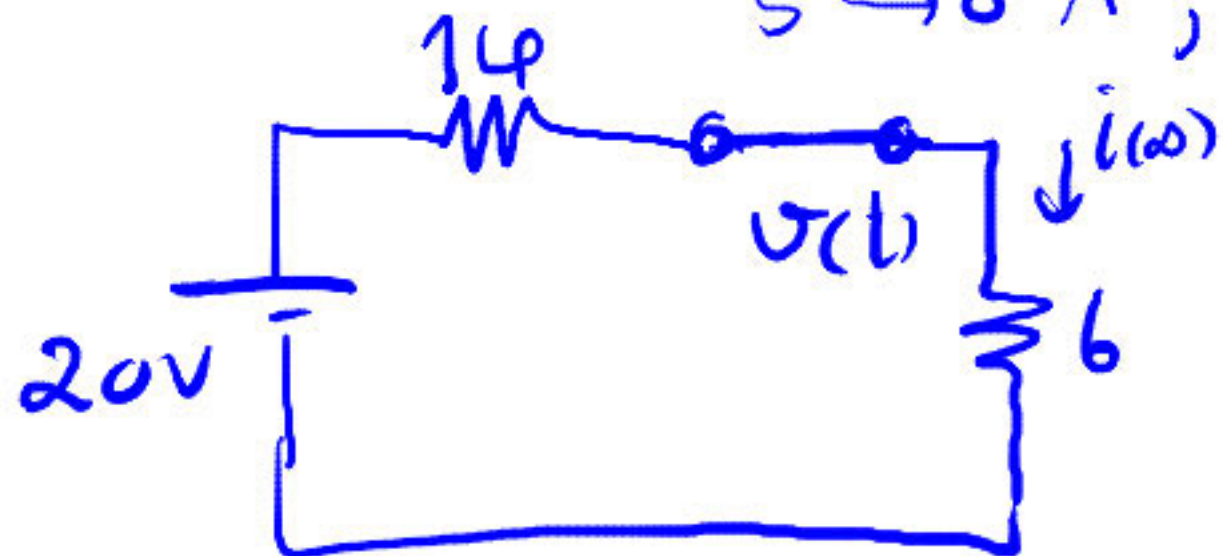
$$5 \rightarrow 0 \text{ A, } v(\infty) = 0$$



$$i(\infty) = \frac{20}{20} = 1 \text{ A}$$

Step ⑤

$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}; t > 0$$

$$= 0 + [-80 - 0] e^{-t/0.2}; t > 0$$


$$= -80 e^{-t/0.2} = -80 e^{-5t} \text{ V.}; t > 0$$

$$i(t) = 1 + [5 - 1] e^{-t/\tau} = 1 + 4 e^{-t/0.2}$$

$$= 1 + 4 e^{-5t} \text{ A}$$

โจทย์

เวลา i_1 และ i_2 นี้น $t > 0$

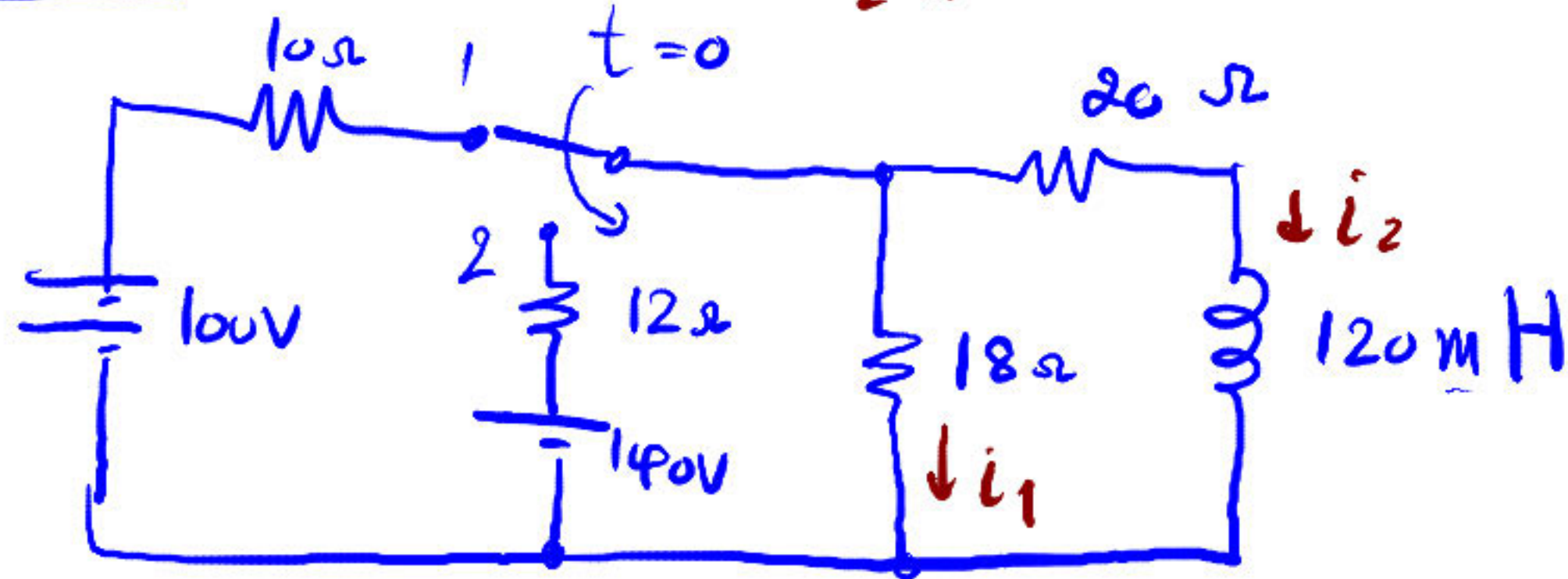


Step 1) หา $\tau = L_{eq}/R_{eq}$ นี้น $t > 0$

$$\tau = \frac{120 \times 10^{-3}}{21.47}$$




Step 2

$i_1(0^-)$, $i_2(0^-)$

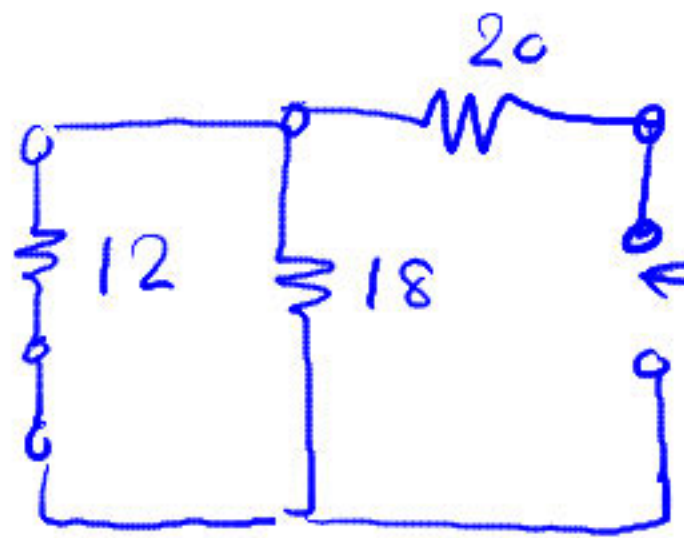

$$R_{eq} = (12 // 18) + 20$$

Step ②

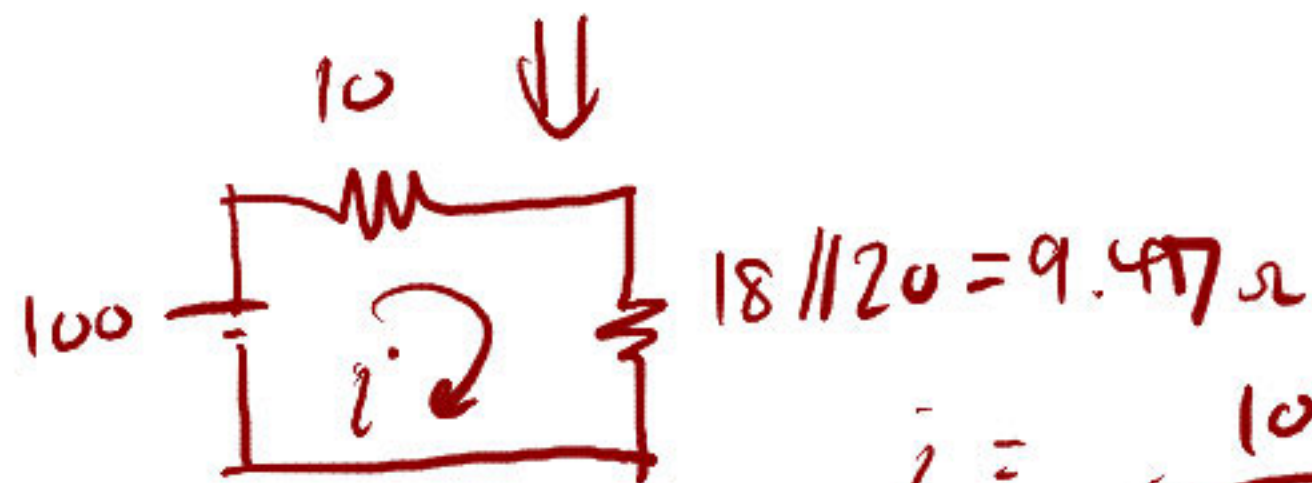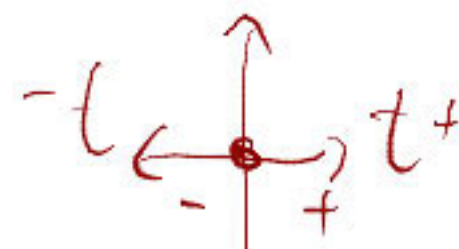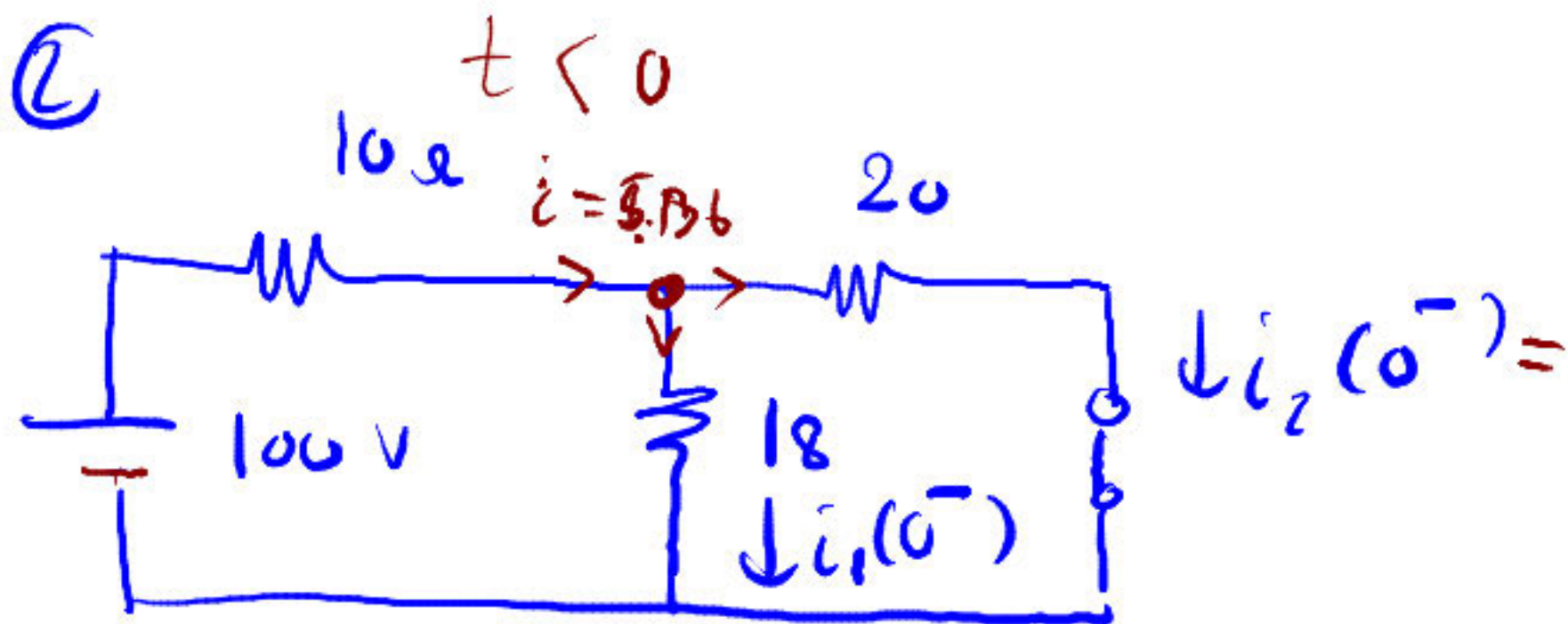

$$18 \parallel 20 = 9.477 \Omega$$

$$\bar{i} = \frac{100}{10 + 9.477} = 5.136 \text{ A}$$


$$i_1(0^-) = 5.136 \left(\frac{20}{20 + 18} \right) = 2.7 \text{ A}$$

$$i_2(0^-) = 5.136 \left(\frac{18}{20 + 18} \right) = 2.43 \text{ A}$$

$$i_1(t) = i_1(\infty) + [i_1(0^+) - i_1(\infty)] e^{-t/\tau}; t > 0$$


$$3.43 + [2.7 - 3.43] e^{-t/5.58 \times 10^{-3}} \text{ A}$$

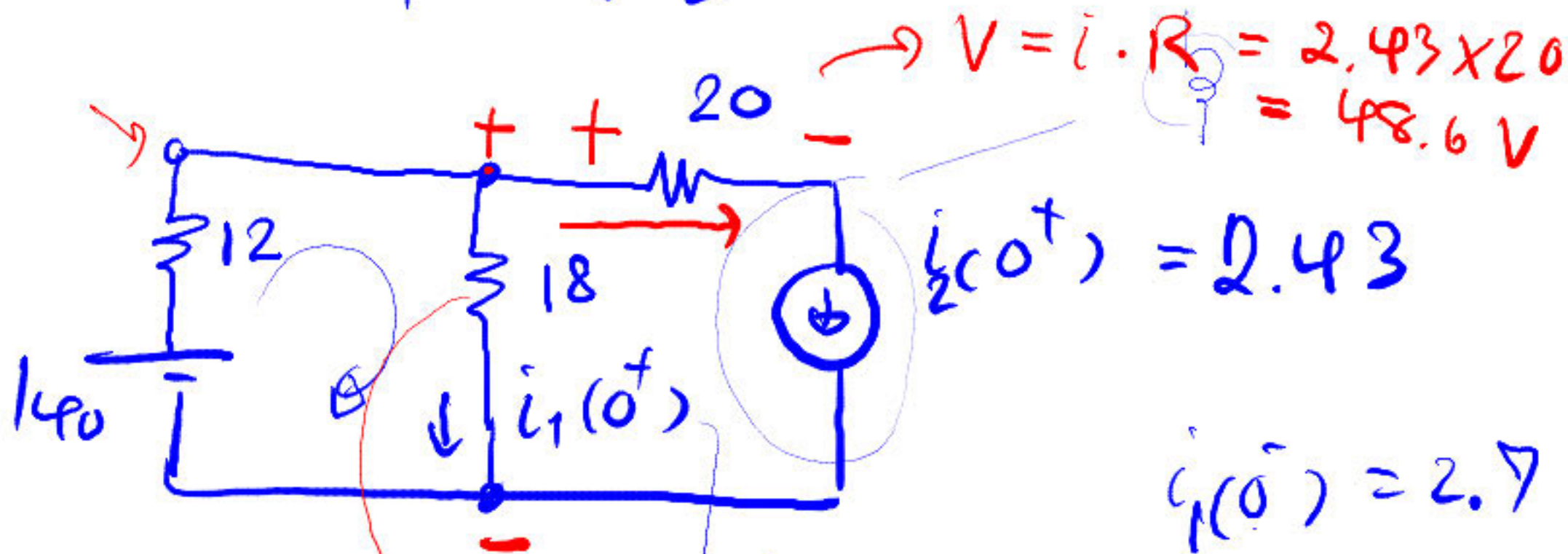Step ③ for $i_1(0^+)$, $i_2(0^+)$: $t > 0$




$$i_1(0^+) = \frac{48.6}{18} = 2.7 \text{ A}$$



Step ④ $t = \infty$

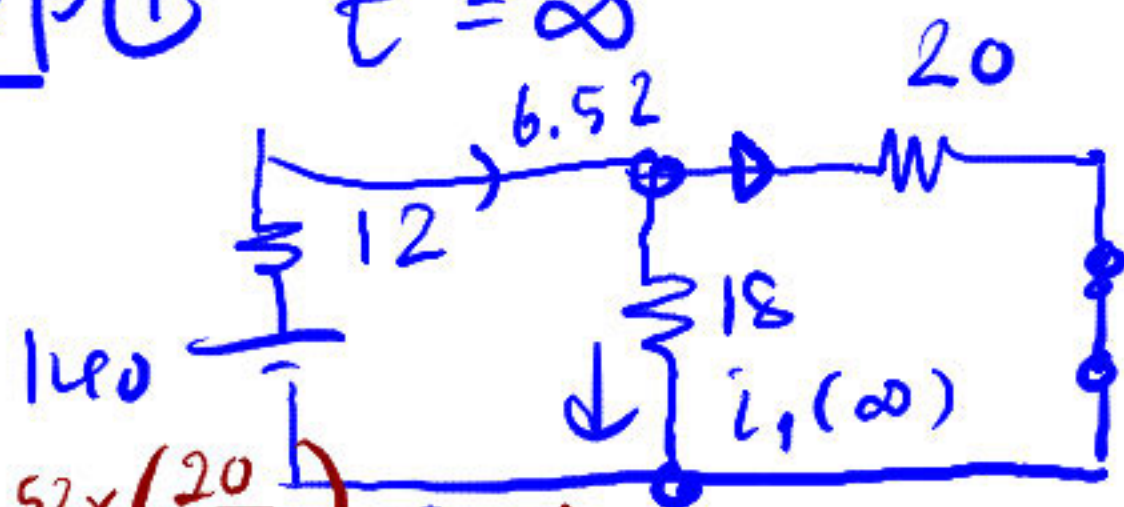

$$i_1(\infty) = 6.52 \times \left(\frac{20}{18+20} \right) = 3.43 \text{ A}$$

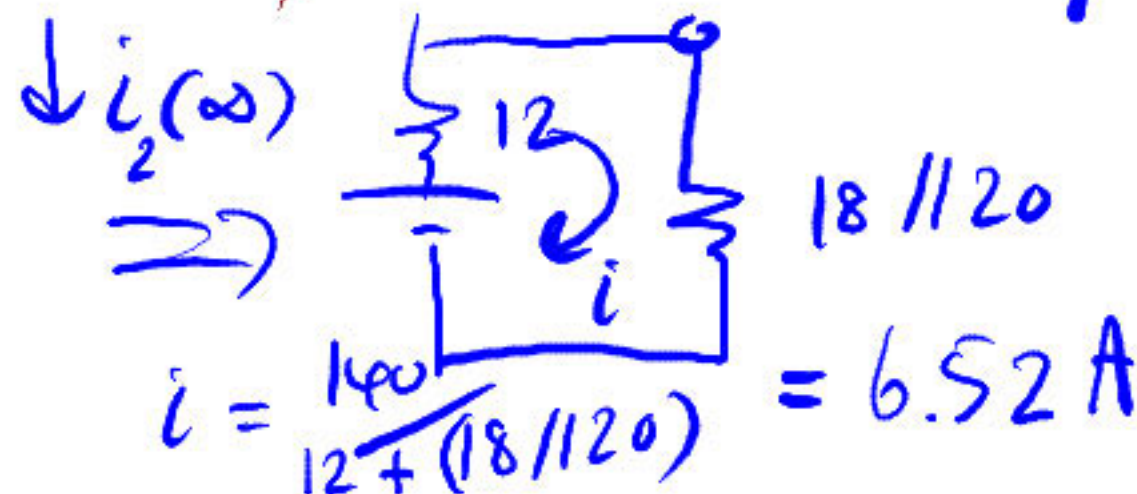
$$6.52 \left(\frac{18}{18+20} \right) = 3.09 \text{ A}$$



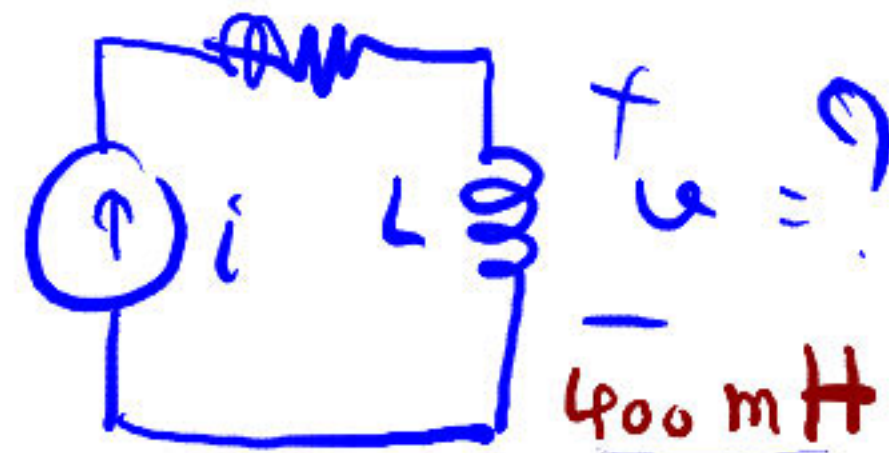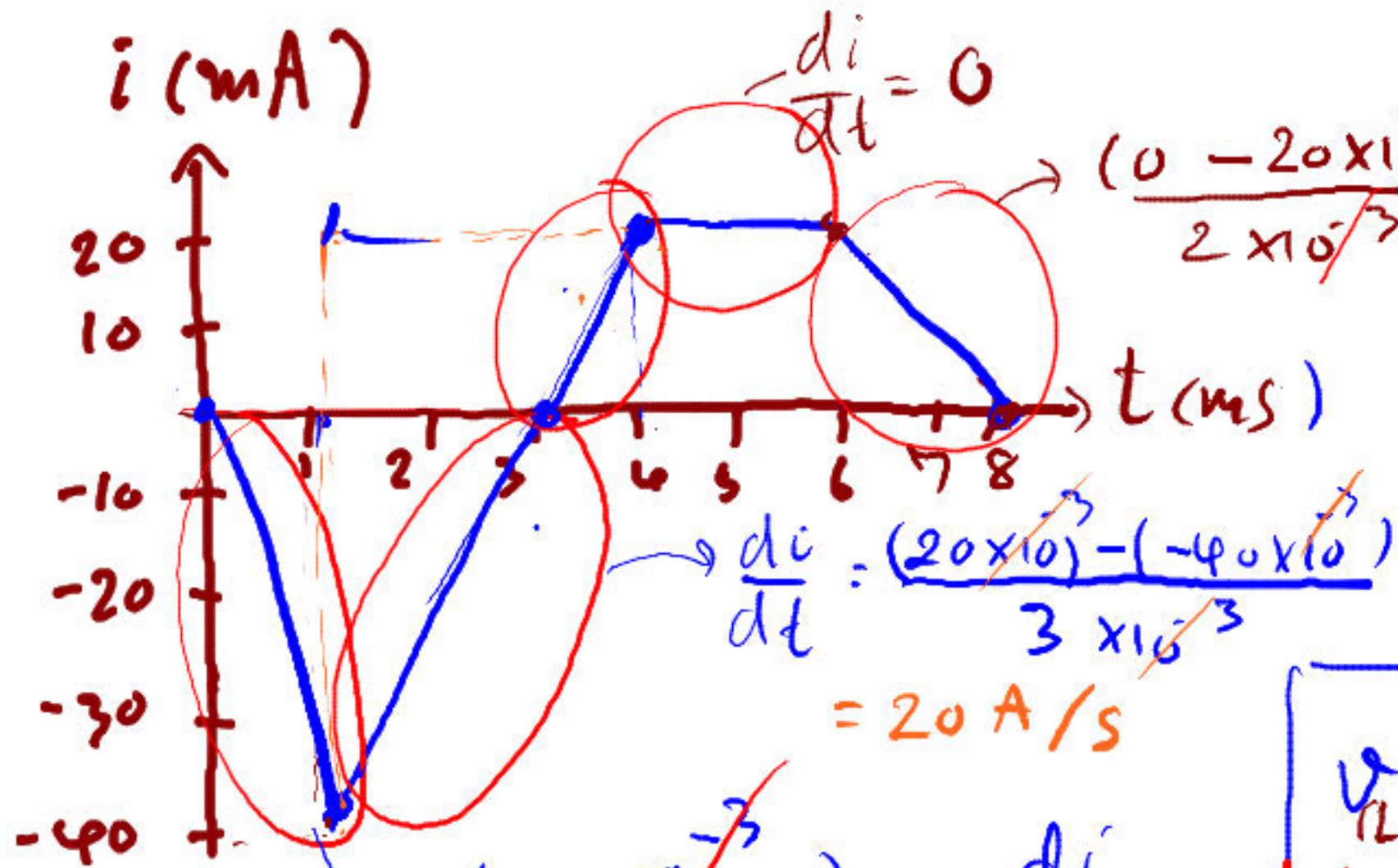

$$v_{(L)} = L \frac{di}{dt} \quad \text{*****}$$

$$t=0, 0 < t < 1 \Rightarrow v = ?$$

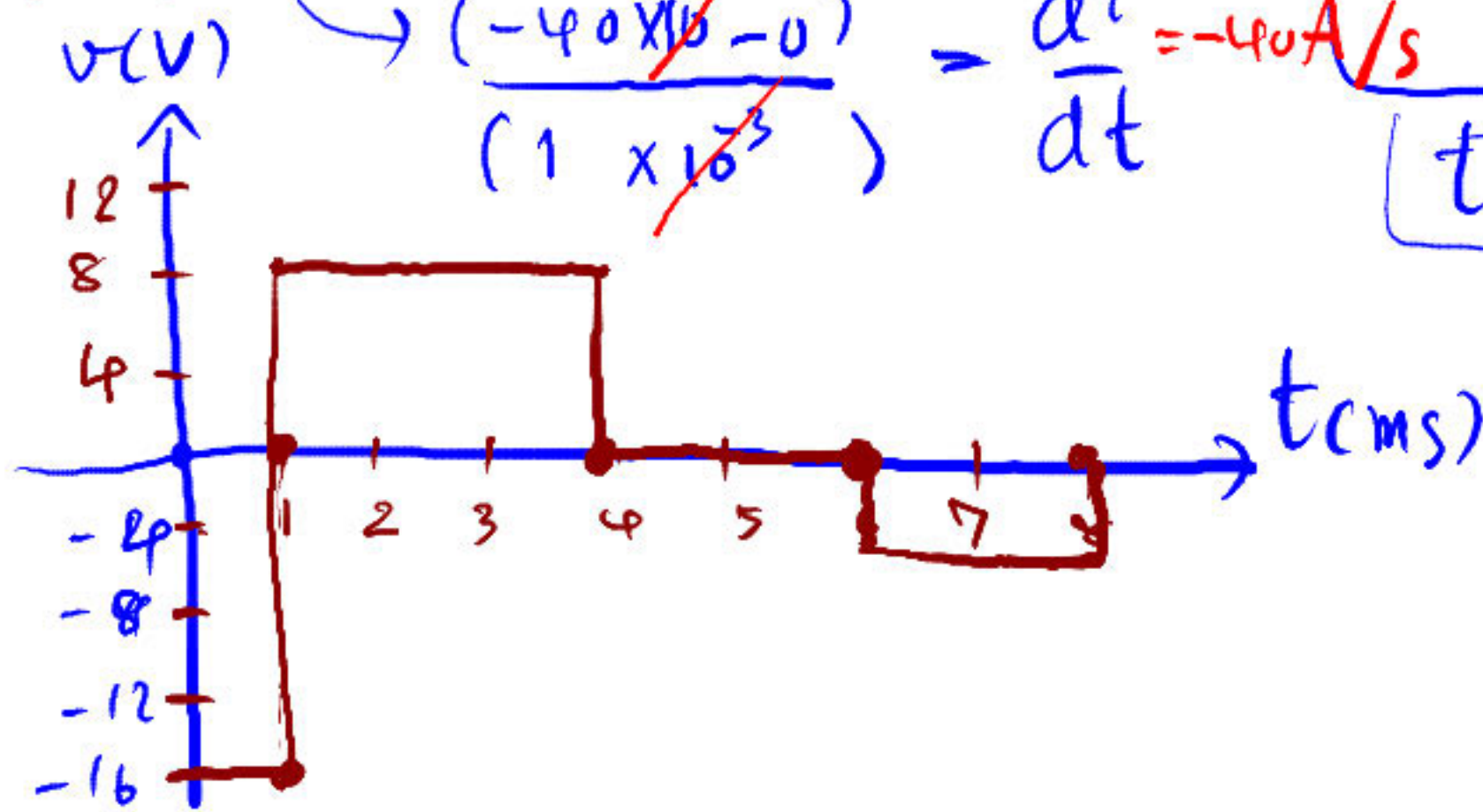

$$v = 400 \times 10^{-3} \times (-40)$$

$$= -16 \frac{\text{H} \cdot \text{A}}{\text{s}} \Rightarrow v$$