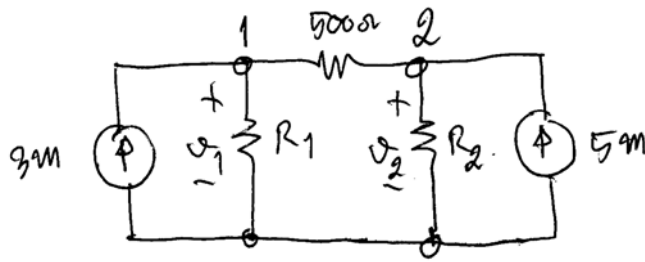


0. nodal #4

①

① in R_1, R_2 $v_1 = 1, v_2 = 2$ volt



Nodal #1; $\frac{v_1}{R_1} + \frac{v_1 - v_2}{500} = 0.003$ — ①


#2; $-\frac{v_1 - v_2}{500} + \frac{v_2}{R_2} = 0.005$ — ②

Do $v_1 = 1V, v_2 = 2V$ in the ① and ②

in ① $\frac{1}{R_1} + \frac{(1-2)}{500} = 0.003$
 $R_1 = \frac{1}{0.003 + \frac{1}{500}} = 200\Omega$

in ② $-\frac{1+2}{500} + \frac{2}{R_2} = 0.005$
 $R_2 = \frac{2}{0.005 + \frac{1}{500}} = 667\Omega$

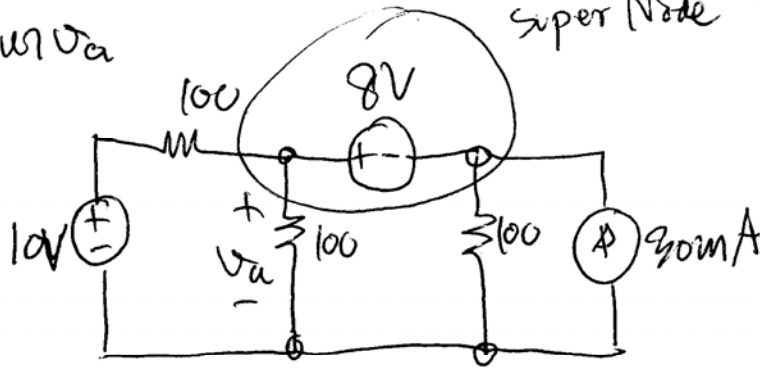Q. Find V_a Super Node $8V \rightarrow 0$ Q.



KCL supernode

$$\frac{V_a - 10}{100} + \frac{V_a}{100} + \frac{V_a - 8}{100} = 0.03 \text{ A}$$


$$\frac{V_a}{100} - \frac{10}{100} + \frac{V_a}{100} + \frac{V_a - 8}{100} = 0.03 \text{ A}$$


$$\frac{3V_a}{100} = 0.03 + \frac{10}{100} + \frac{8}{100}$$

$$V_a = \frac{100(0.03 + \frac{10}{100} + \frac{8}{100})}{3}$$

$$= \frac{3 + 10 + 8}{3} = 7 \text{ Volt}$$

Sim by Tina

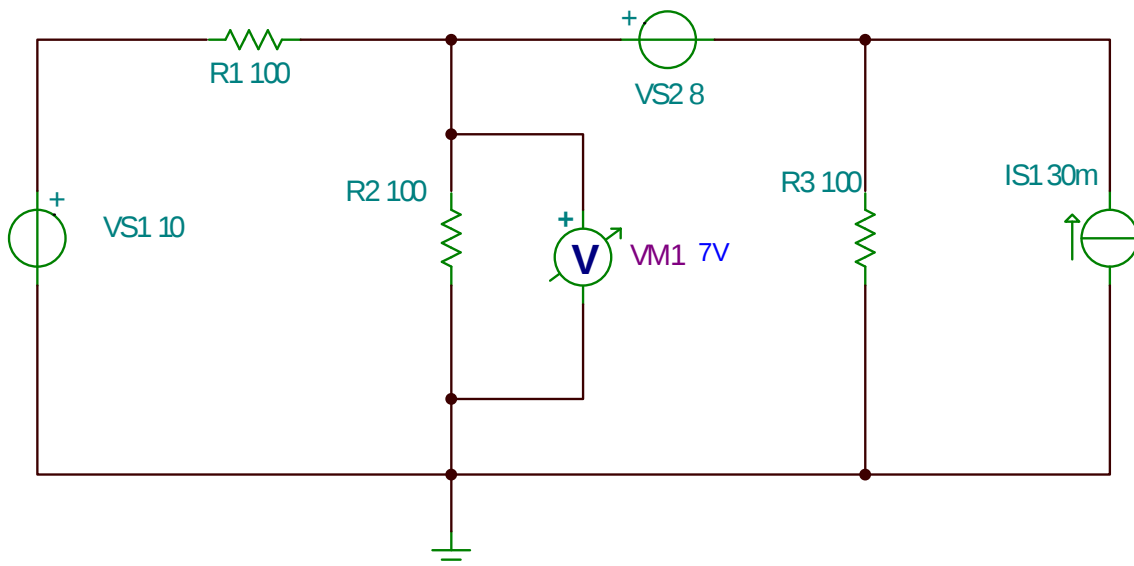

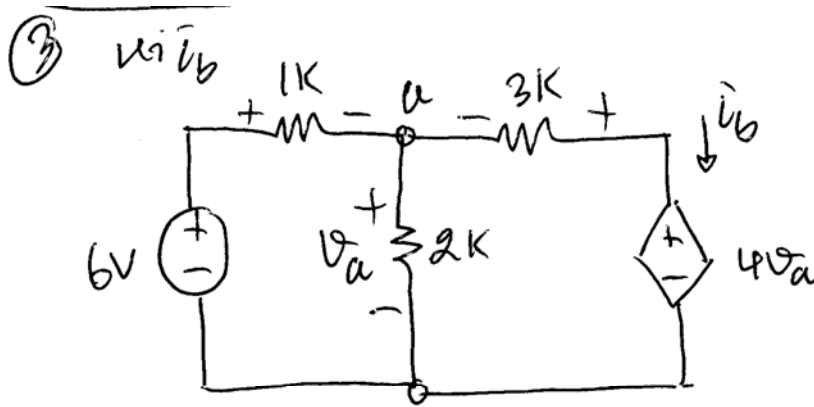


Transforms Node a.

$$\frac{V_a - 6}{1000} + \frac{V_a}{2000} + \frac{V_a - 4V_a}{3000} = 0$$

$$V_a = 12V$$


$$\therefore i_b = \frac{V_a - 4V_a}{3000} = -12mA$$

Sim by Tina

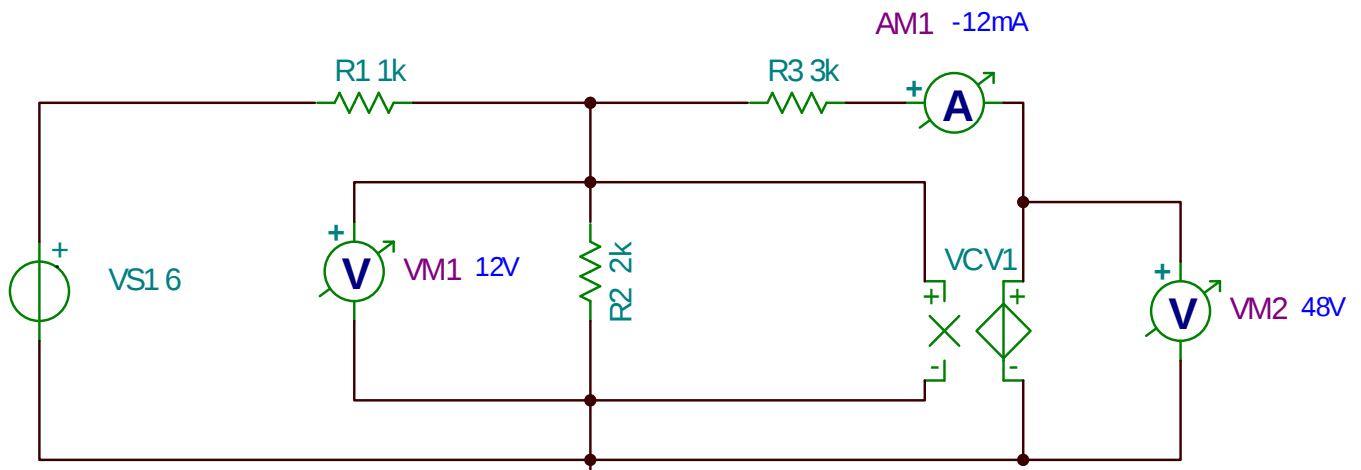

(3)

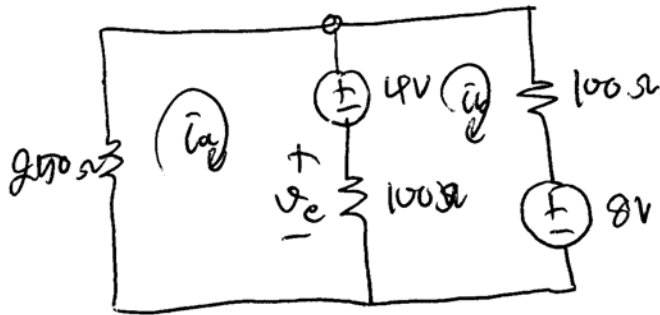(904) ឱរក $\bar{v}_a$ និង $\bar{v}_b$ ទំនាក់ទំនង 120



Mesh #1 $\Rightarrow$ KVL:

$$250 \bar{i}_a - 100 \bar{v}_b + 4V = 0$$

$$250 \bar{v}_a - 100 \bar{v}_b = -4 \quad \text{--- (1)}$$


Mesh #2 $\Rightarrow$ KVL:

$$-100 \bar{v}_a + 200 \bar{v}_b - 4 + 8 = 0$$

$$-100 \bar{v}_a + 200 \bar{v}_b = -4 \quad \text{--- (2)}$$


$$\begin{bmatrix} 250 & -100 \\ -100 & 200 \end{bmatrix} \begin{bmatrix} \bar{v}_a \\ \bar{v}_b \end{bmatrix} = \begin{bmatrix} -4 \\ -4 \end{bmatrix}$$
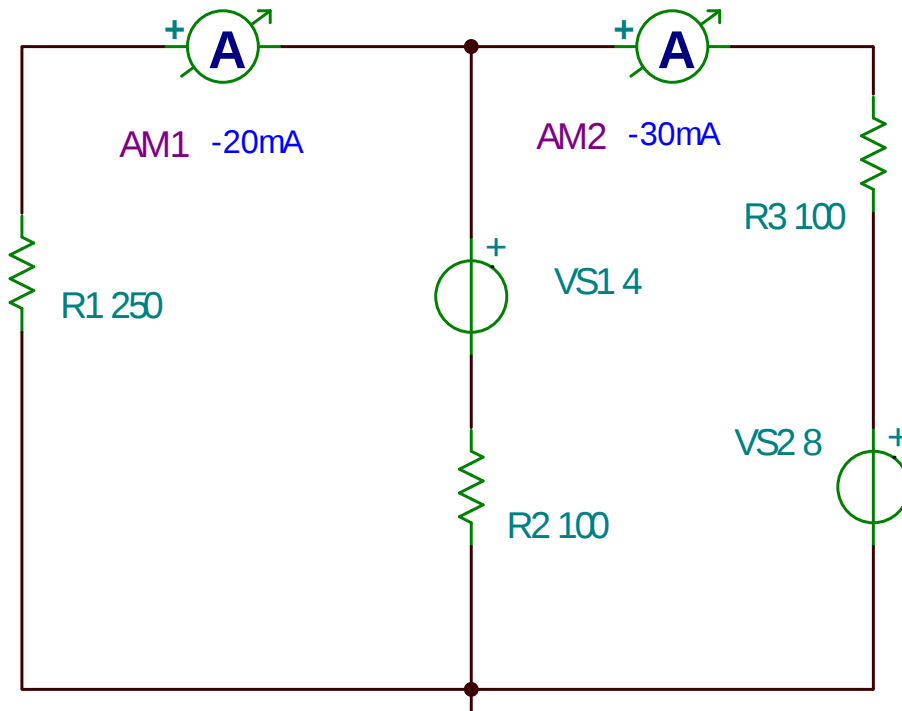
$$\begin{bmatrix} \bar{v}_a \\ \bar{v}_b \end{bmatrix} = \begin{bmatrix} 250 & -100 \\ -100 & 200 \end{bmatrix}^{-1} \begin{bmatrix} -4 \\ -4 \end{bmatrix} = \begin{bmatrix} -0.02 \\ -0.03 \end{bmatrix}$$



905. $V_0 = 50V_0$

④

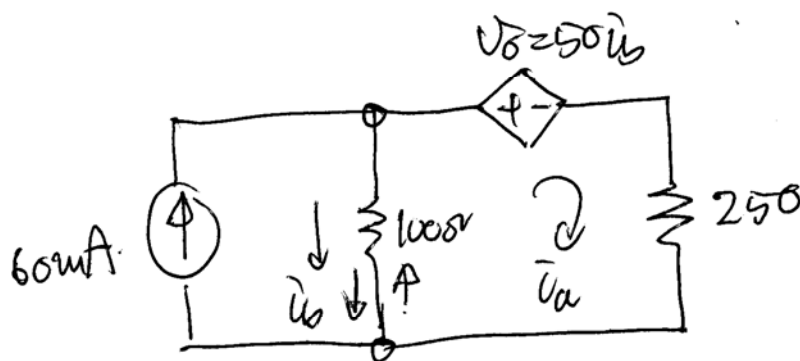

$$i_b = 60mA - i_a \quad \text{--- (1)}$$

KVL mesh m:

$$-100(0.06 - i_a) + 50(0.06 - i_a) + 250i_a = 0$$

$$i_a = 10mA$$

$$\begin{aligned} \text{Hence } V_0 &= 50i_b = 50(0.06 - 0.01) \\ &= 2.5 \text{ Volt} \end{aligned}$$

